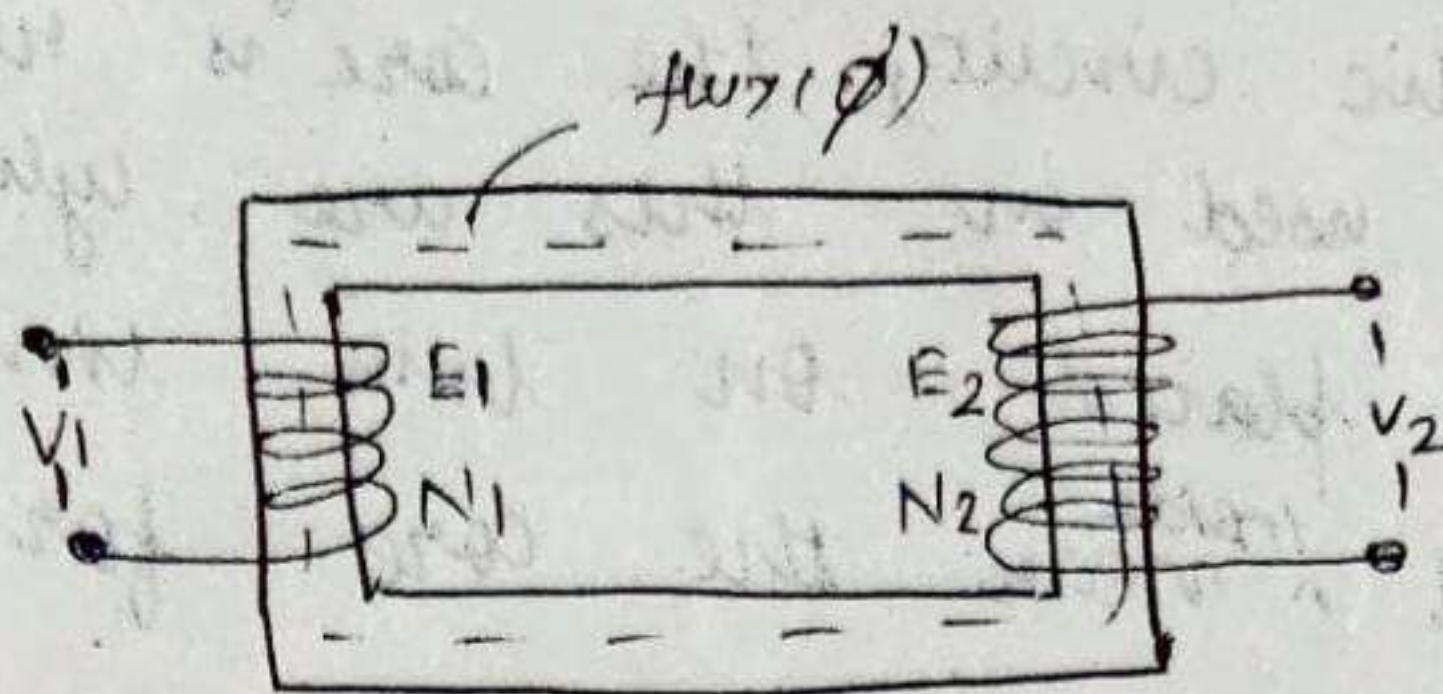


* EMF EQUATION OF TRANSFORMER-

$\phi_m = \text{max flux}$

(9)



Let V_1 = AC voltage applied to primary of the T/F

ϕ = Alternating flux produced

N_1 = No. of turns in primary wdg


N_2 = No of turns in secondary wdg

E_1 = EMF induced in Primary due to alternating flux (ϕ)

E_2 = EMF induced in Secondary due to " "

f = supply frequency

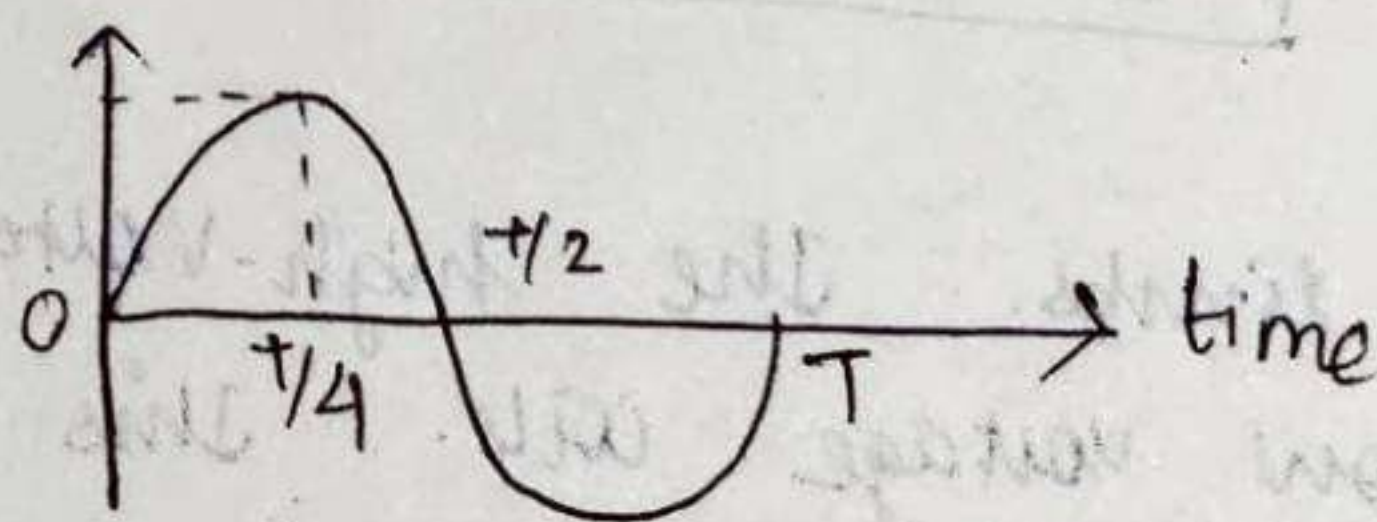- We know from Faraday's law of electromagnetic induction
- Average emf induced per turn = $\frac{d\phi}{dt}$
- Consider $\frac{1}{4}$ th cycle of flux -



- Average emf per turn = $\frac{\text{Change in flux}}{\text{Change in time}}$

$$\begin{aligned} \text{So, average emf per turn} &= \frac{\phi_m - 0}{T/4 - 0} \\ &= \frac{4\phi_m}{T} \end{aligned}$$

$$\text{Average emf per turn} = 4f\phi_m \quad \therefore \text{as } T = \frac{1}{f}$$

W-

$$\text{Form factor} = \frac{\text{RMS value of EMF}}{\text{Average value of EMF}} = 1.11$$

$$\begin{aligned} \text{So, RMS value of emf per turn} &= \text{Av. emf} \times 1.11 \\ &= 4f\phi_m \times 1.11 \\ &= 4.44f\phi_m \end{aligned}$$

Total emf induced in N_1 turns

$$E_1 = 4.44f\phi_m N_1 \text{ Volt} \quad \text{--- (1)}$$

Total emf induced in N_2 turns of secondary

$$E_2 = 4.44f\phi_m N_2 \text{ Volt} \quad \text{--- (2)}$$

From (1) & (2)

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} \quad \text{--- (3)}$$

Now,

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

and

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = K$$

then,

$$K = \frac{N_2}{N_1}$$

and

$$K = \frac{E_2}{E_1}$$

K is Transformation ratio

Note-

- (a) Step-up T/F $\Rightarrow N_2 > N_1$
- (b) Step-down T/F $\Rightarrow N_2 < N_1$
- (c) Isolation T/F $\Rightarrow N_2 = N_1$

* IDEAL TRANSFORMER-

Properties-

- It will have no losses
- It's winding Resistance will be Zero
- It's leakage flux will be zero
- Very small current is required to produce flux.
- There is no voltage drop in primary

→ Note:-

$$V_1 = E_1$$

$$V_2 = E_2$$


$$\frac{E_2}{E_1} = \frac{V_2}{V_1} = k$$

$$V_1 I_2 = I_1 V_2$$

↓

$$\frac{E_2}{E_1} = \frac{V_2}{V_1} = \frac{I_1}{I_2} = k \rightarrow \text{Transformation ratio}$$
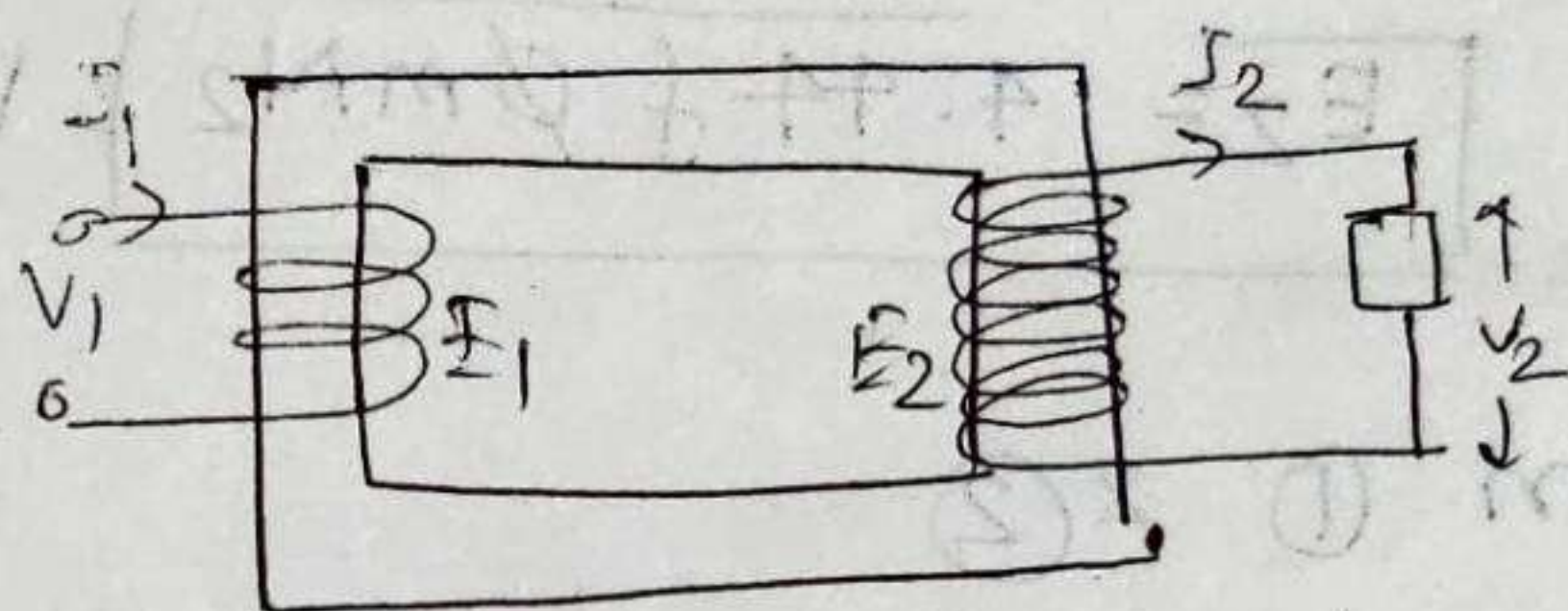
$$\begin{aligned} \rightarrow E_2 &= k E_1 \\ \rightarrow V_2 &= k V_1 \\ \rightarrow I_2 &= I_1 / k \end{aligned}$$



$$\frac{E_1}{N_1} = \frac{E_2}{N_2}$$

$$k = \frac{E_2}{E_1}$$


* KVA RATING OF T/F-

In transformers, ratings are given in KVA becoz power consumption in transformer is due to the following reasons:-


- Copper loss
- Iron loss

* PRACTICAL TRANSFORMER - (on no load) -

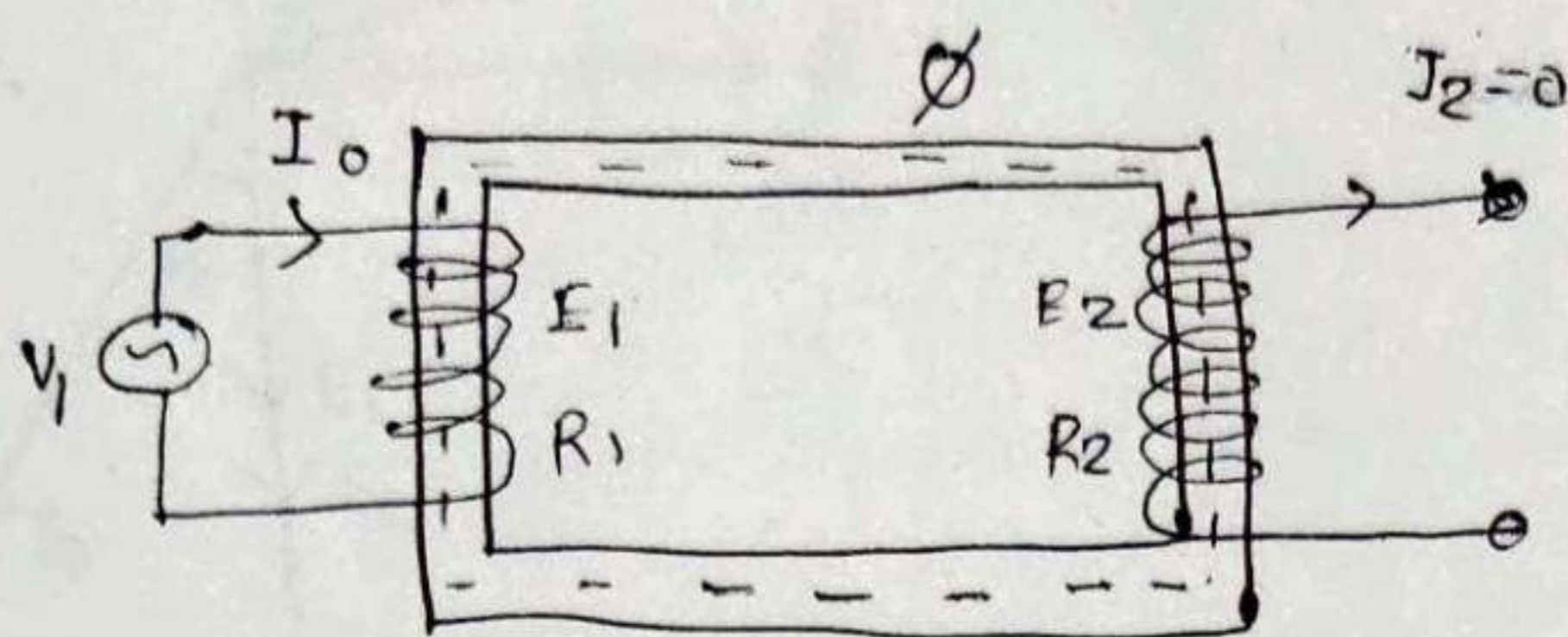In practical T/F primary winding has some resistance. So, primary coil will have inductance as well as Resistance.



Phasor diagram

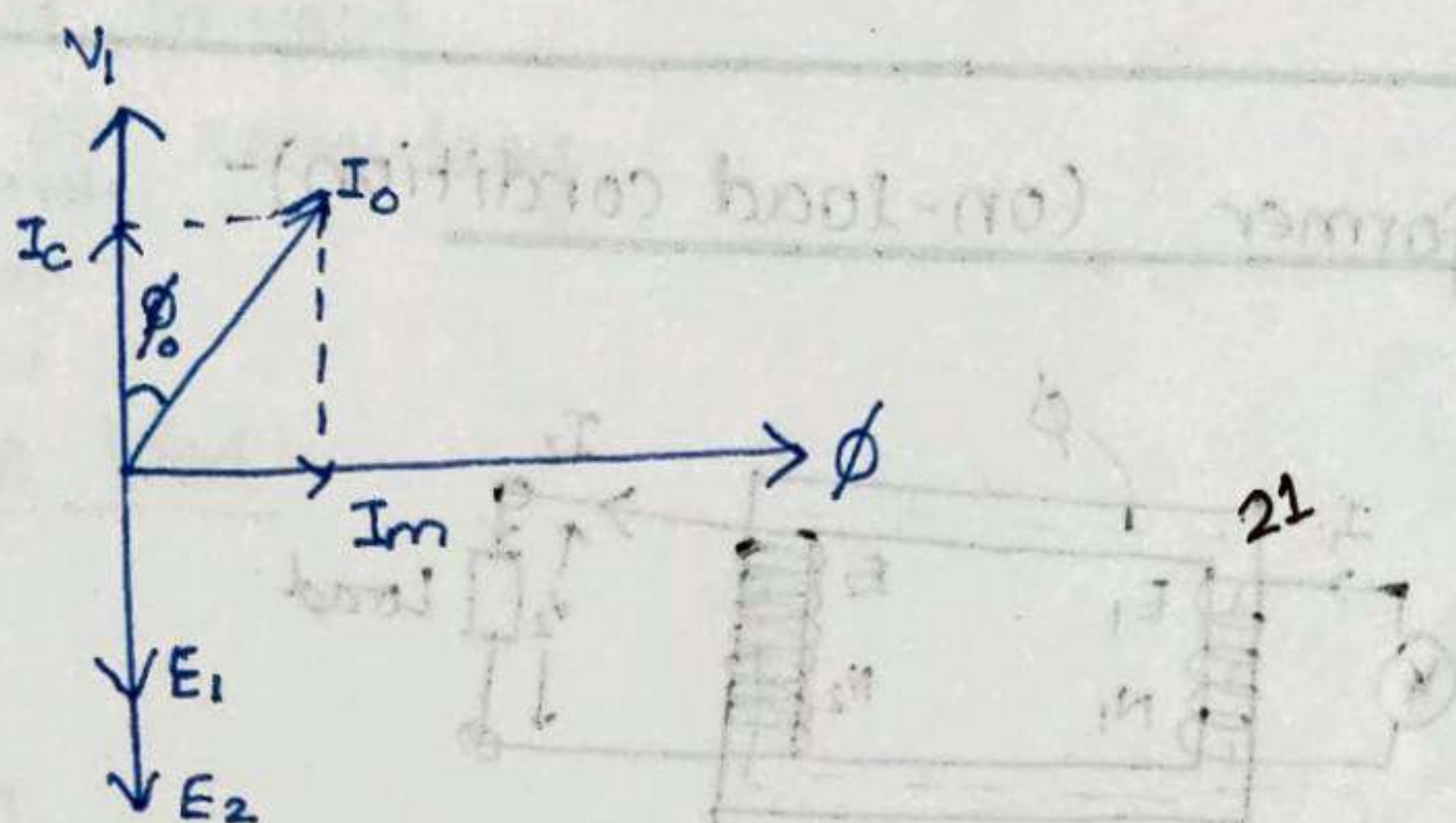

- ϕ_0 = no load phase angle
- I = no load current
- B/W V & I current is not 90° .

$$\boxed{I_0^2 = I_m^2 + I_c^2}$$

→ I_m = magnetising current (magnetised core or generation of flux)

→ I_c = core loss current

$$\vec{I}_0 = \vec{I}_m + \vec{I}_c$$

$$\boxed{I_c = W_{core} + W_{cu}}$$

→ W_{cu} is very small due to small no load current.

→ $I_c \cong W_{core \text{ loss}}$ (neglecting W_{cu})

$$\therefore \boxed{I_c = W_{core \text{ loss}}}$$

$$\rightarrow I_c = I_0 \cos \phi_0$$

$$\rightarrow I_m = I_0 \sin \phi_0$$

No load power loss formula -

$$\boxed{W_0 = V I_0 \cos \phi_0}$$

- $I_0 = 3\% - 5\%$ of full load (I_{fl})

- Flux pass through core

- $\phi = \frac{MMF (NI)}{S}$

$$NI = \phi S$$

$\rightarrow \phi$ is constant.


$$NI \propto S$$

$$\boxed{I_0 \propto S}$$

- $R = \rho \frac{l}{A}$

- $S = \frac{l}{\mu_r A}$

◎ Ideal transformer (on-load condition)-

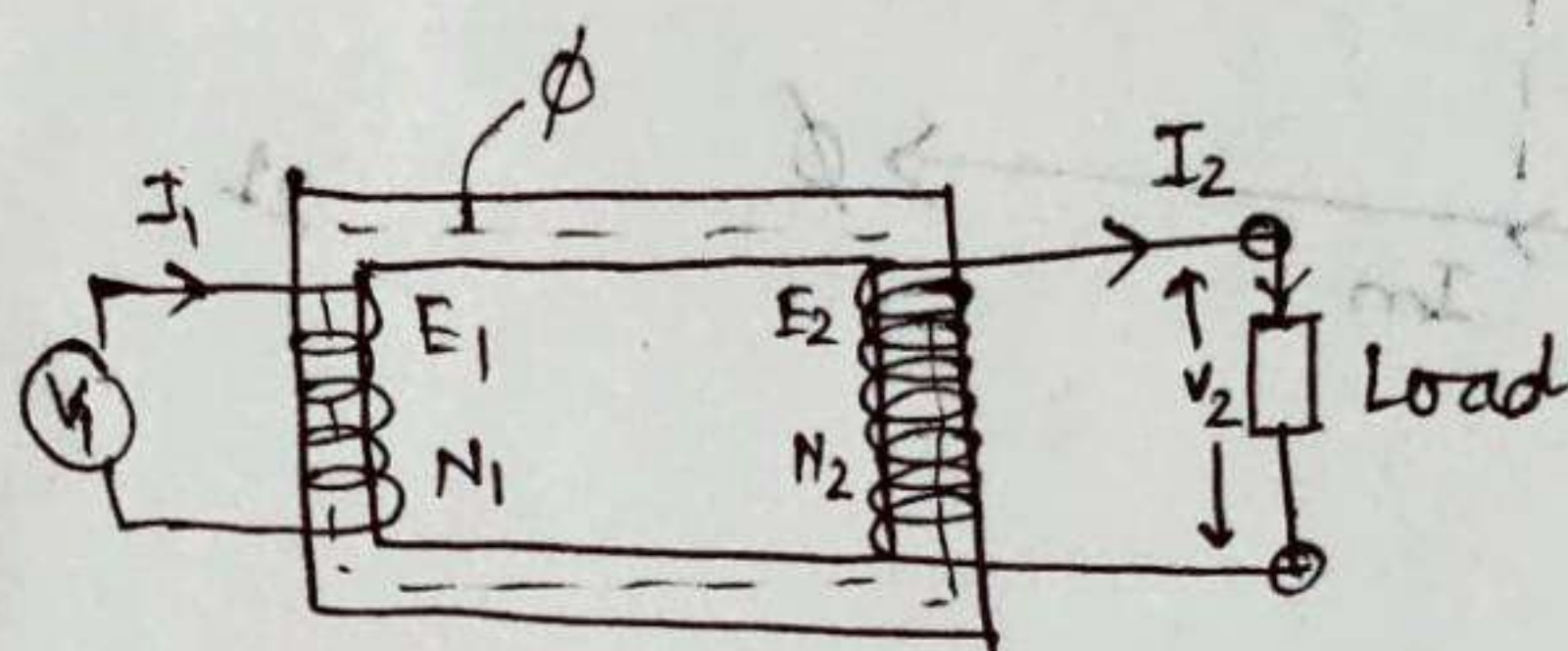

Here resistance is very low or negligible that's why it's a ideal transformer condition

Here $\rightarrow$

- I_1 = current drawn from primary coil under load condition
- I_2 = current in the secondary drawn by load in the secondary coil







- $\boxed{\bar{I}_1 = \bar{I}_0 + \bar{I}_2'}$

- $\underline{I_2'} = KI_2$ and I_2' is always is antiphase of I_2


Phasor diagram-

Phasor diagram of T/F under on load condⁿ depends up the load power factor.

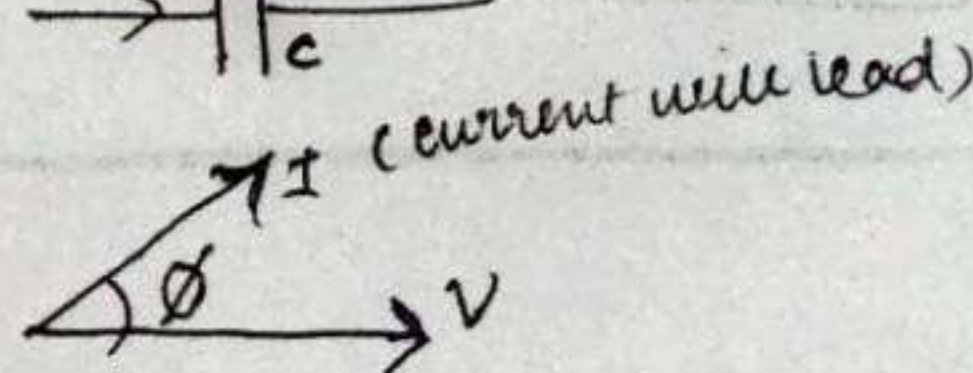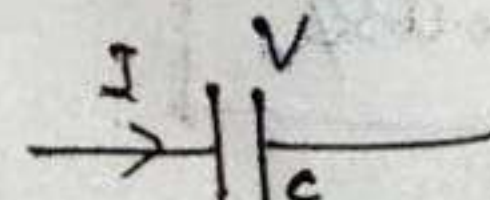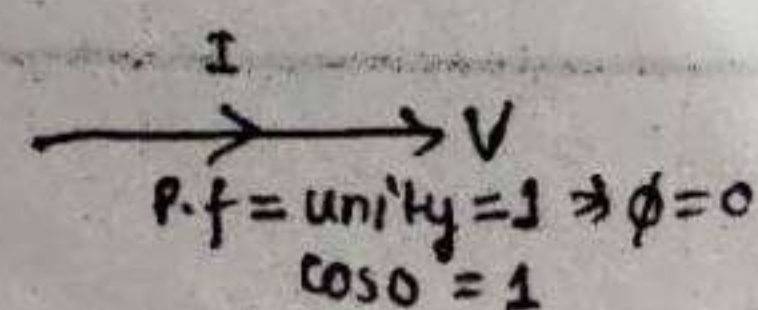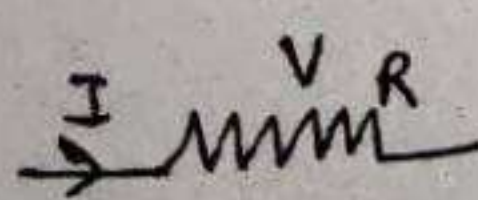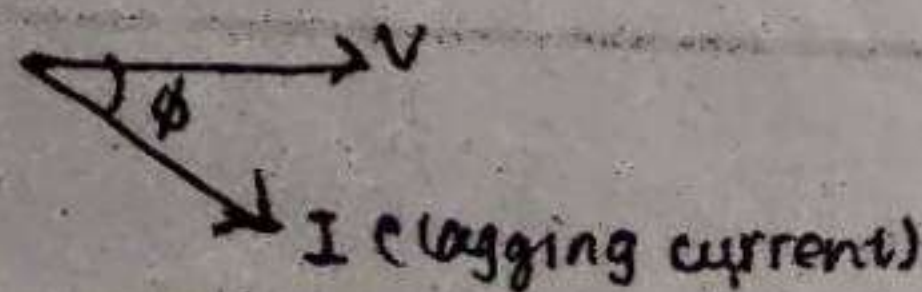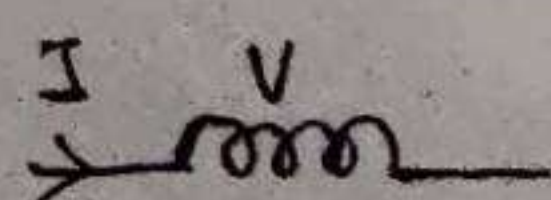- Inductive load $\rightarrow$ coil
- Resistive load $\rightarrow$ Resistance
- Conductive load $\rightarrow$ Conductance plates




(i) For inductor load-

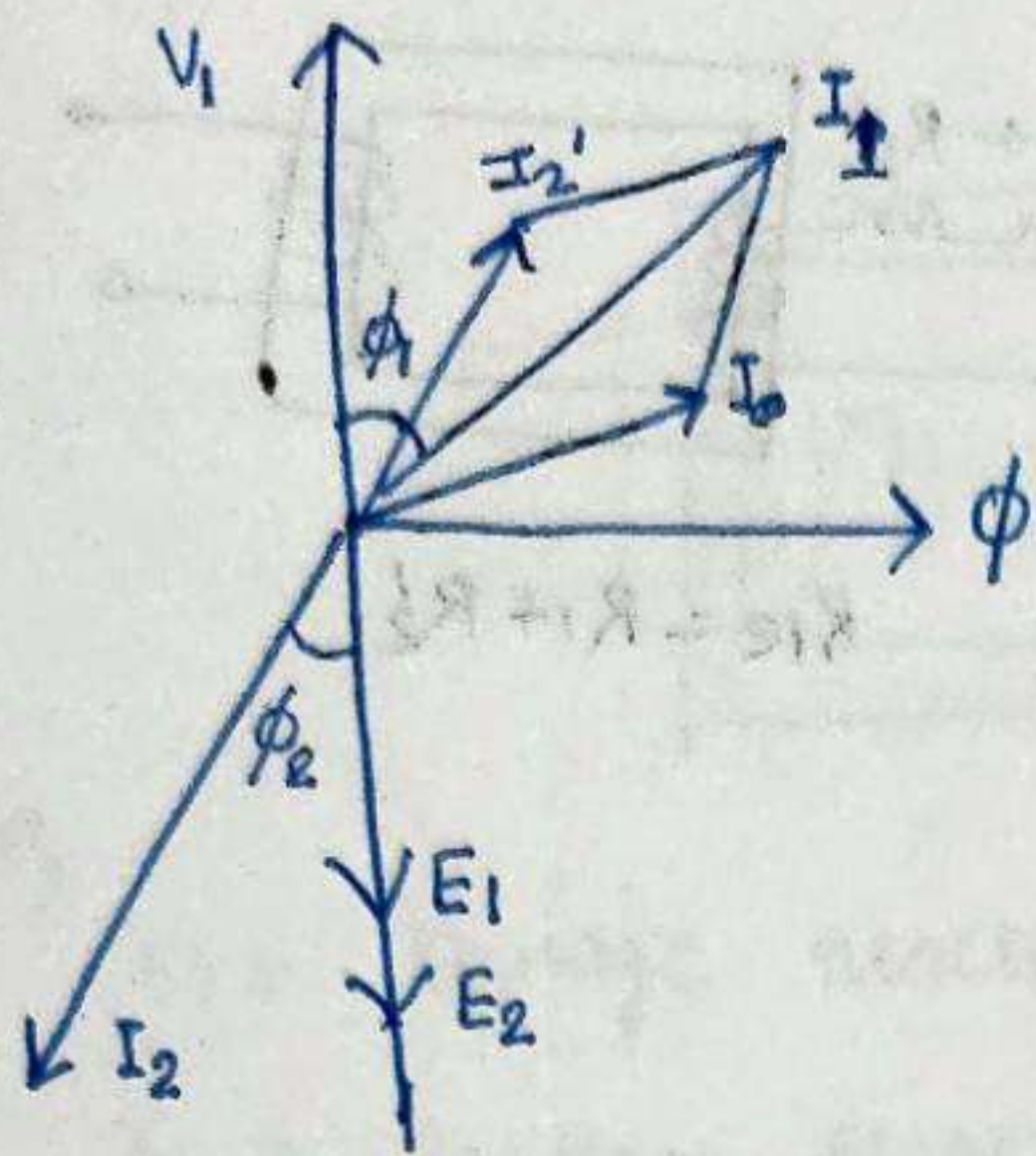

$$\vec{I}_1 = \vec{I}_0 + \vec{I}_2'$$

Note - I_2 will lag $V_2 \& E_2$
 $\phi_1 \rightarrow$ Pf of primary
 $\phi_2 \rightarrow$ Pf of secondary


(ii) For capacitive load-

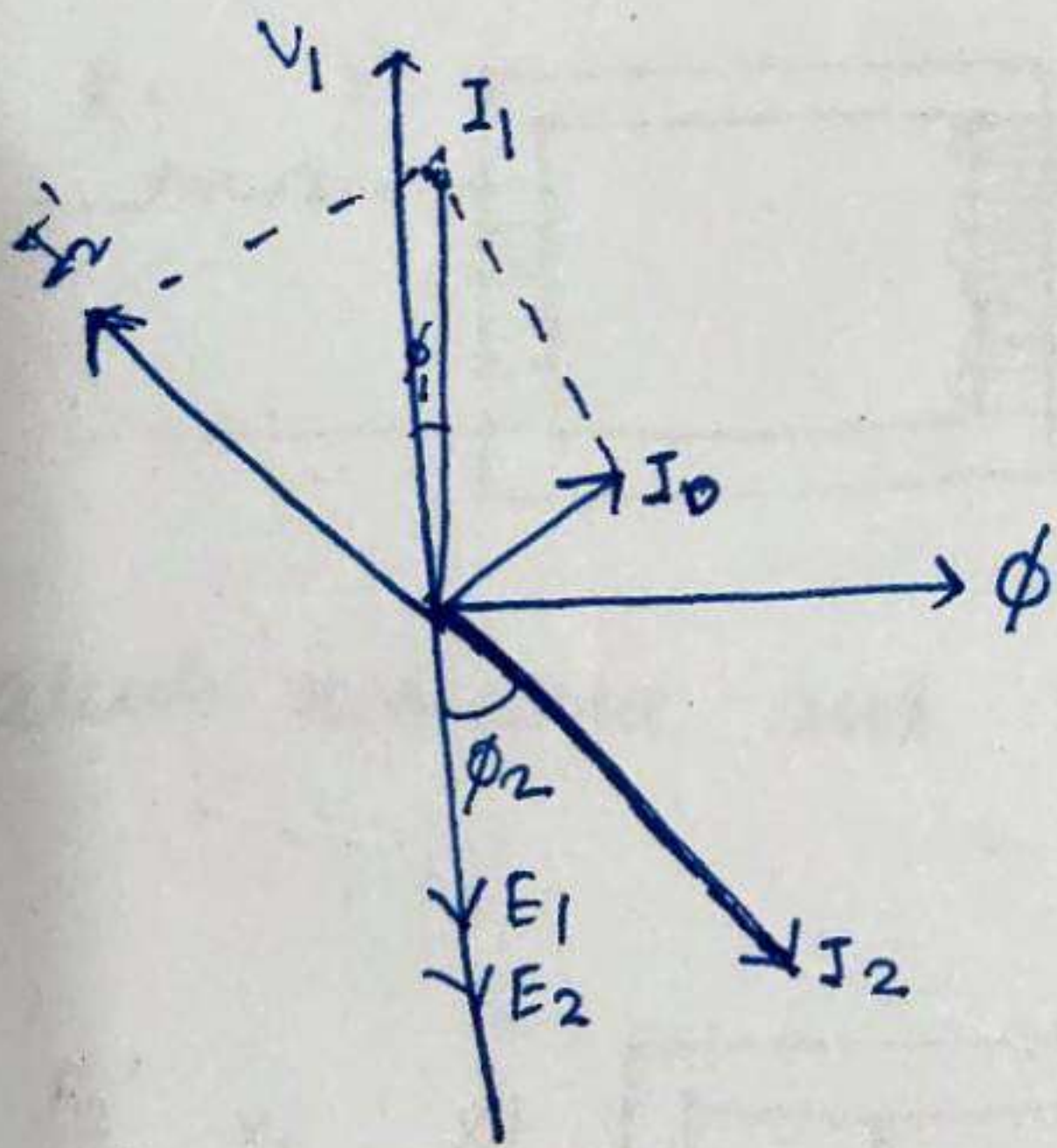

$$\vec{I}_1 = \vec{I}_0 + \vec{I}_2'$$

Note - I_2 leads $(E_2 \& V_2)$



(iii) For resistive load-

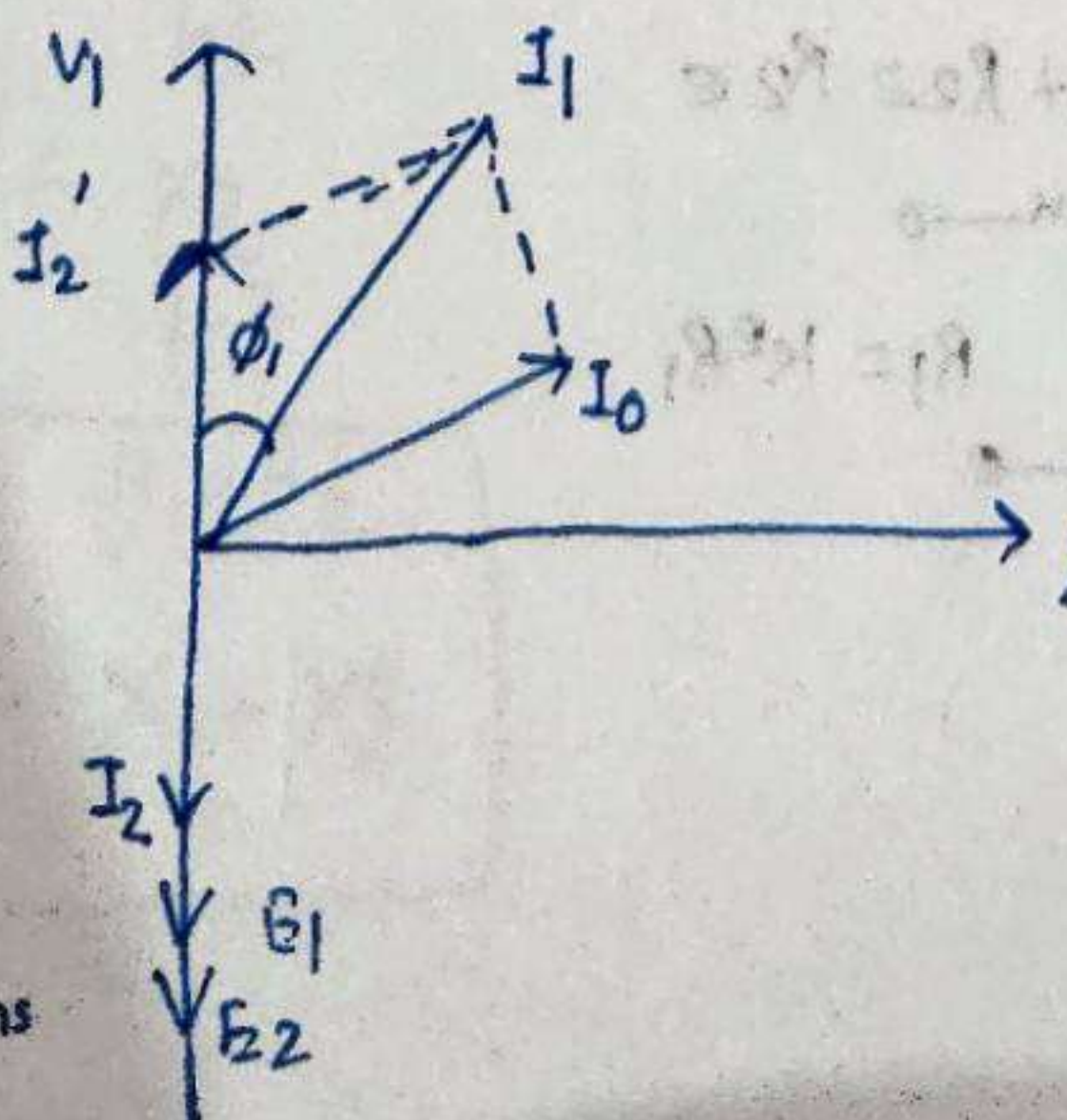

$$\vec{I}_1 = \vec{I}_0 + \vec{I}_2'$$

Note - I_2 will be in phase of $E_2 \& V_2$
 Here, $\phi_2 = 0$, $\cos 0 = 1 \Rightarrow$ it means secondary pf is unity.

* Equivalent Resistance-

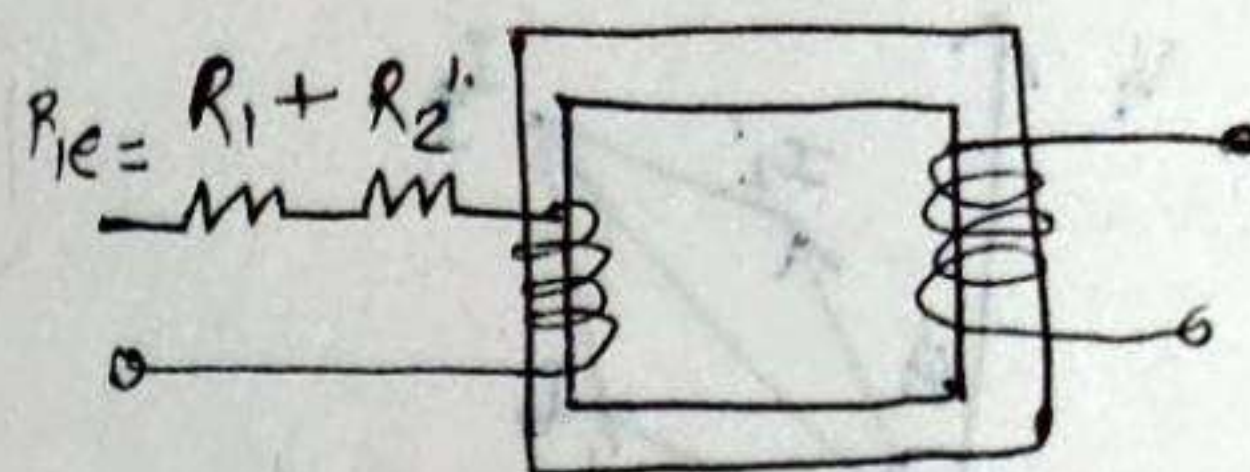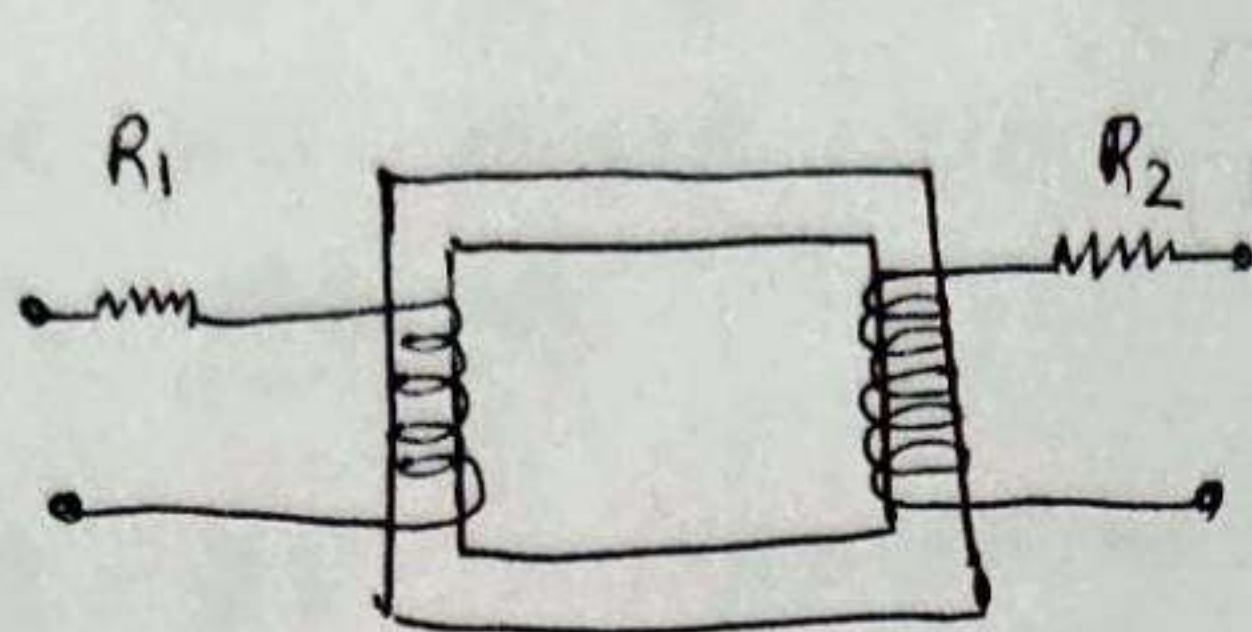

$$R_{1e} = R_1 + R_2'$$

Let,

R_1 = Primary resistance

R_2 = Secondary resistance

R_2' = secondary resistance transferred to primary

$$R_2' = \frac{R_2}{k^2}$$

Total equivalent resistance of the primary $R_{1e} = R_1 + R_2'$


Note-

$$I_1^2 R_2' = I_2^2 R_2$$

$$\frac{I_1^2}{I_2^2} = \frac{R_2}{R_2'}$$

$$k^2 = \frac{R_2}{R_2'}$$


$$R_2' = \frac{R_2}{k^2}$$

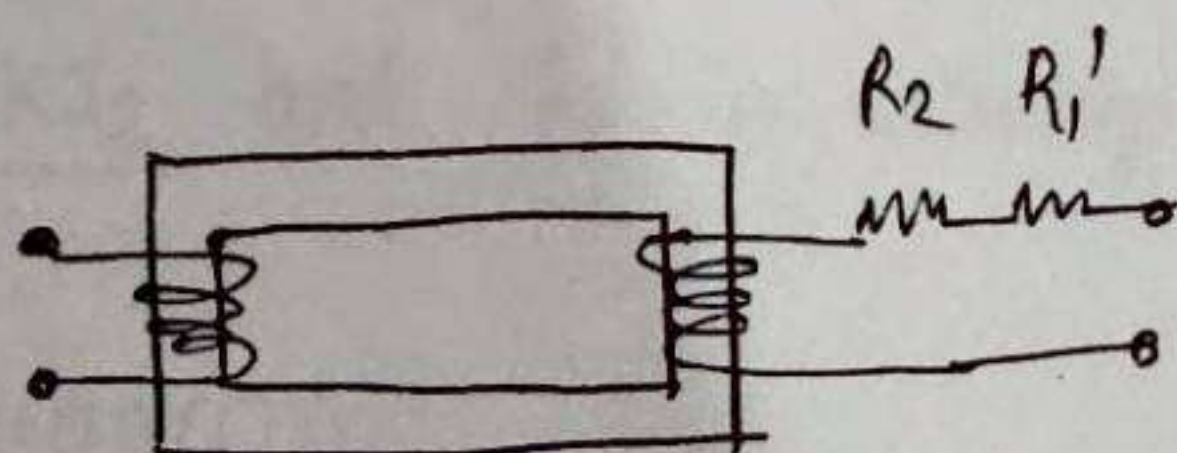

Let,

$$R_1' = R_1 k^2$$

$$R_{2e} = R_2 + R_1'$$

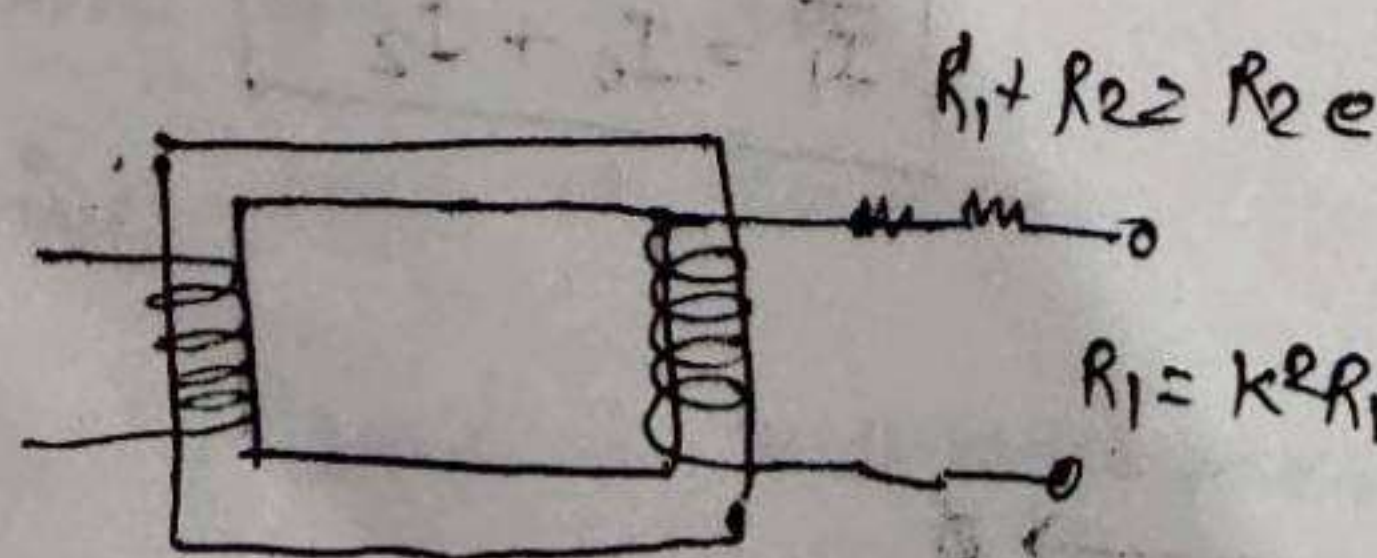


$$R_1' = R_2 = R_{2e}$$

$$R_1 = k^2 R_1'$$

* Reactance of Dyn Transformer (X) -

(12)

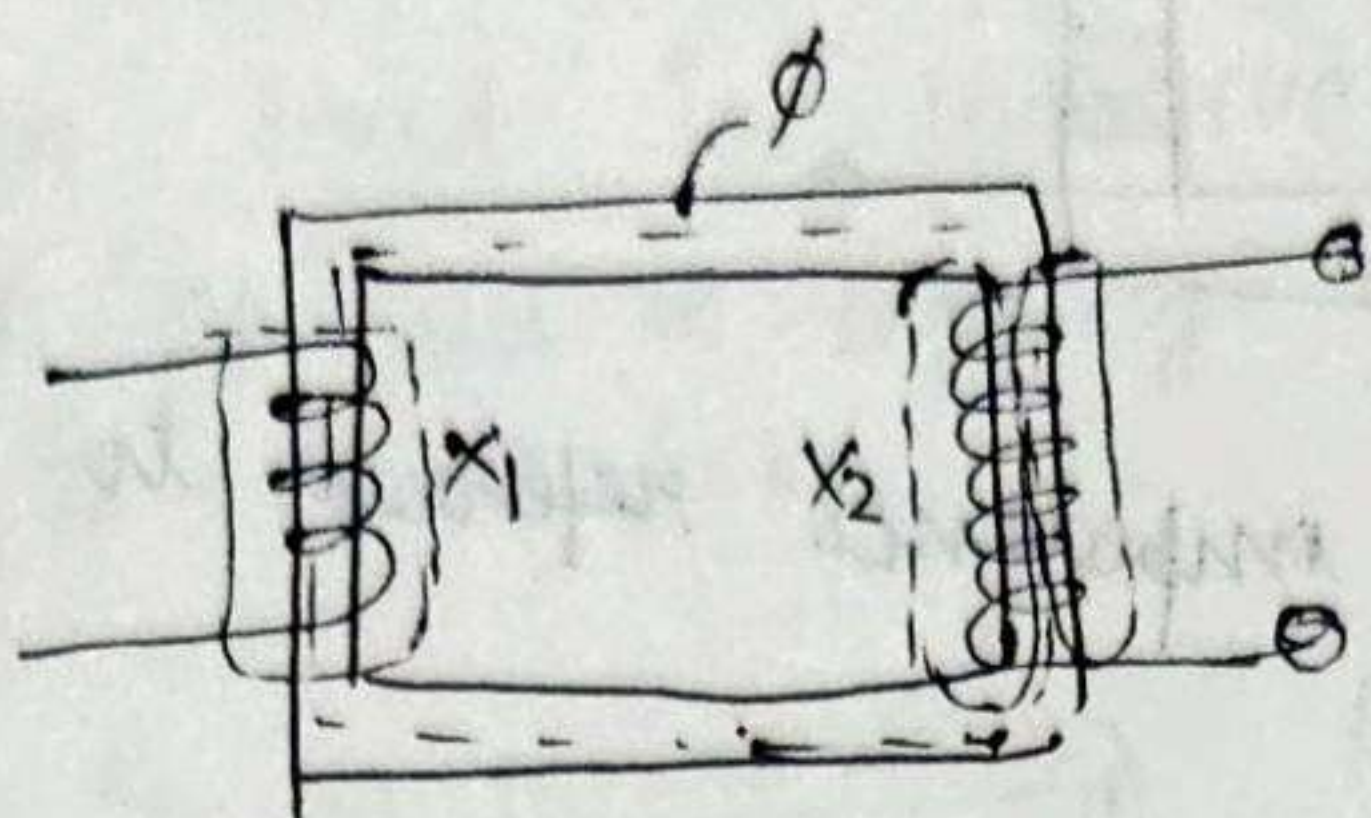

Where,


X_1 = leakage reactance of primary

X_2 = leakage reactance of secondary


$$X_1 = \omega L_1$$

$$X_2 = \omega L_2$$

* Equivalent reactance -

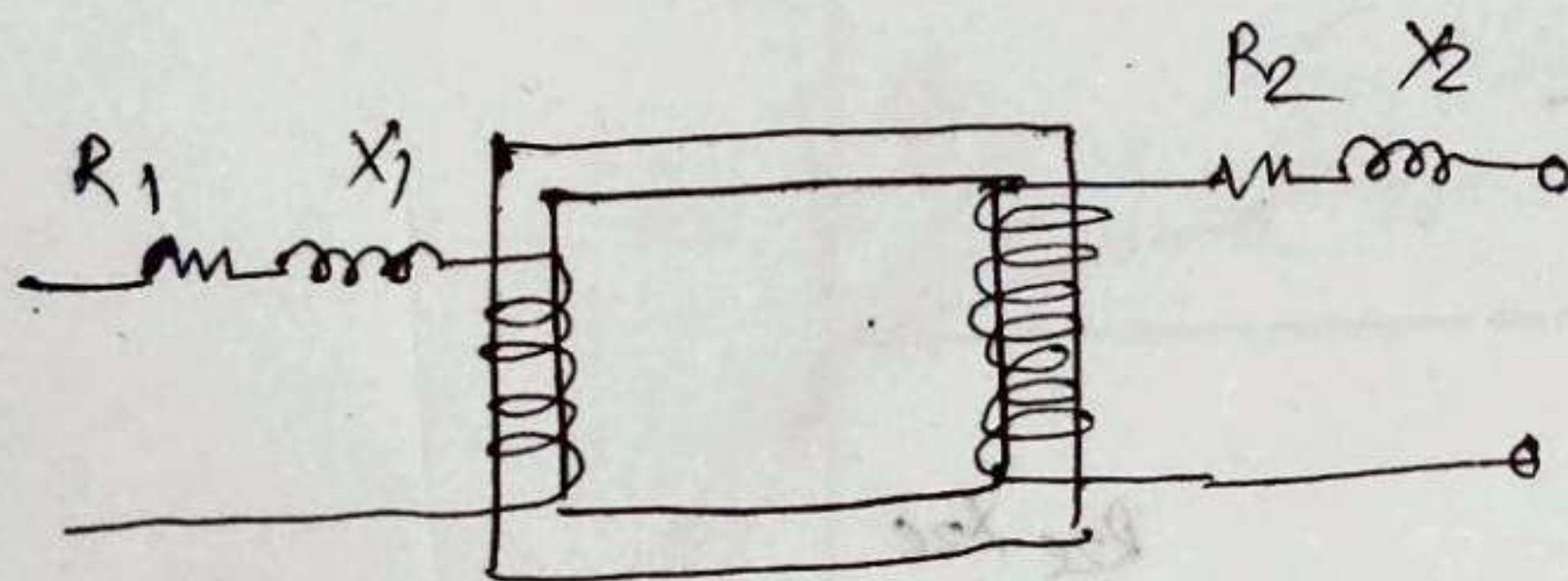

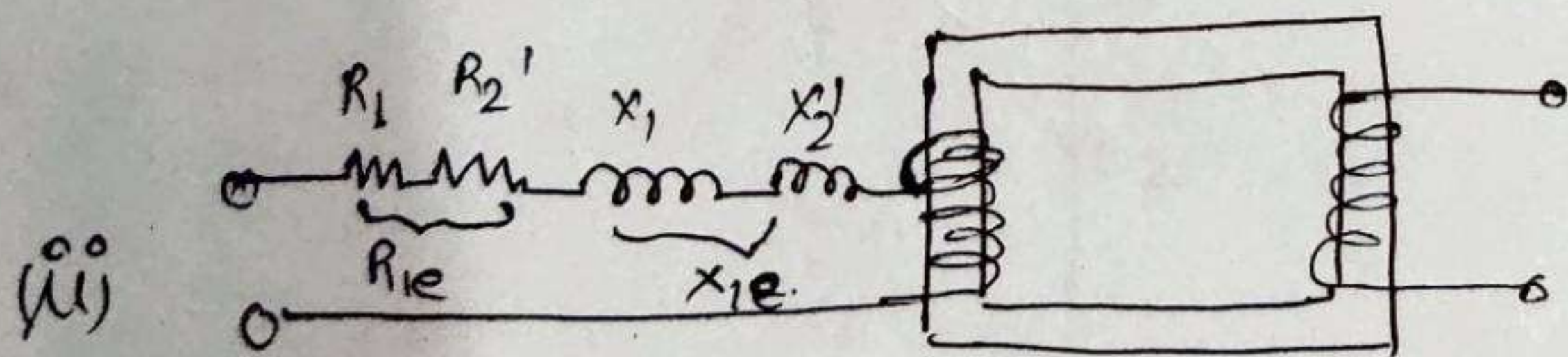Equivalent reactance and resistance on primary side




Here-

$$R_2' = \frac{R_2}{k^2}$$

$$X_2' = \frac{X_2}{k^2}$$

$$R_{ie} = R_1 + R_2'$$

$$X_{ie} = X_1 + X_2'$$

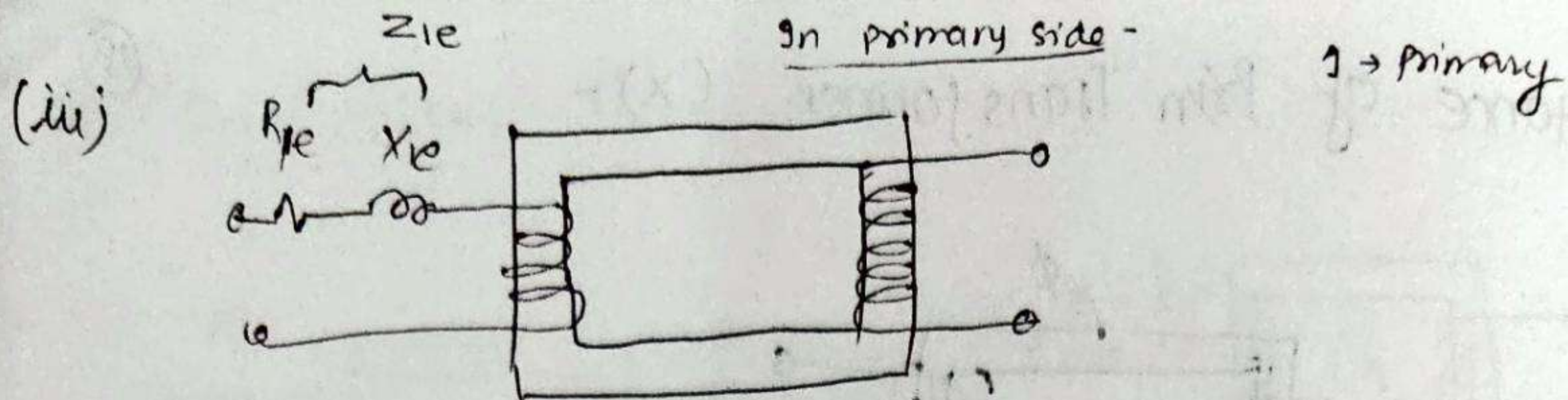

$Z_{1e} \Rightarrow$ Total equivalent impedance referred to primary


$$Z_{1e}^2 = R_{1e}^2 + X_{1e}^2$$

$$Z_{1e} = \sqrt{R_{1e}^2 + X_{1e}^2}$$


$$Z_{1e} = R_{1e} + jX_{1e}$$

In phasor form
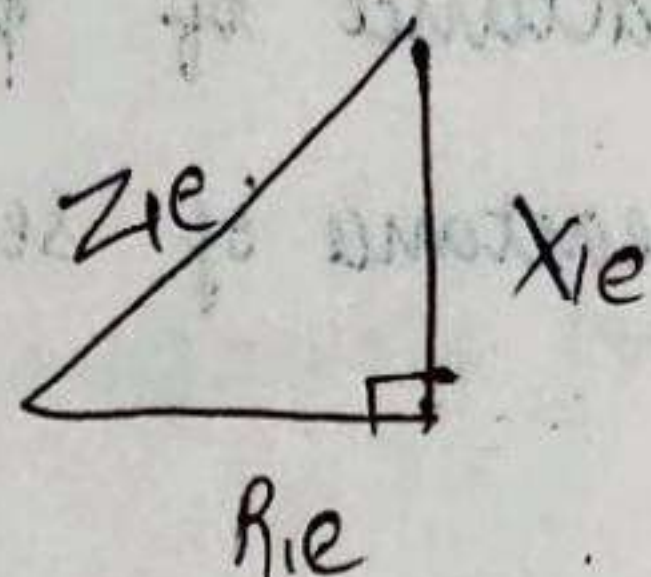
$$\boxed{\bar{Z}_{1e} = \bar{R}_{1e} + j\bar{X}_{1e}}$$



(iv) In Secondary side -

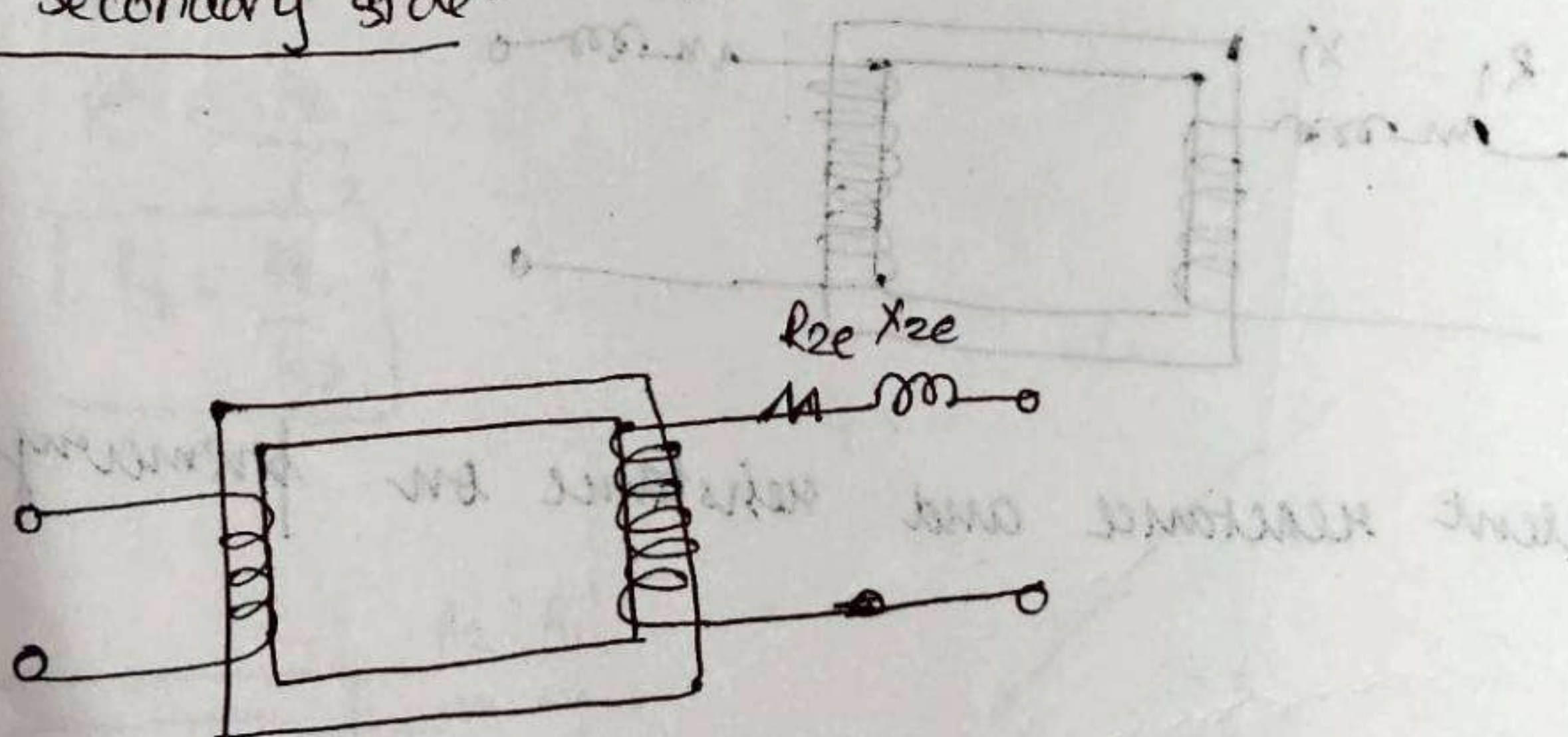

$$R_{2e} = R_2 + R_1'$$

$$= R_2 + K^2 R_1$$

$$X_{2e} = X_2 + X_1'$$

$$= X_2 + K^2 X_1$$

$$\boxed{Z_{2e} = \sqrt{R_{2e}^2 + X_{2e}^2}}$$



$$\boxed{R_{1e} = R_1 + R_2'$$

$$X_{1e} = X_1 + X_2'}$$

* Phasor diagram of T/F on load - (15)

Case (i) When load is inductive -

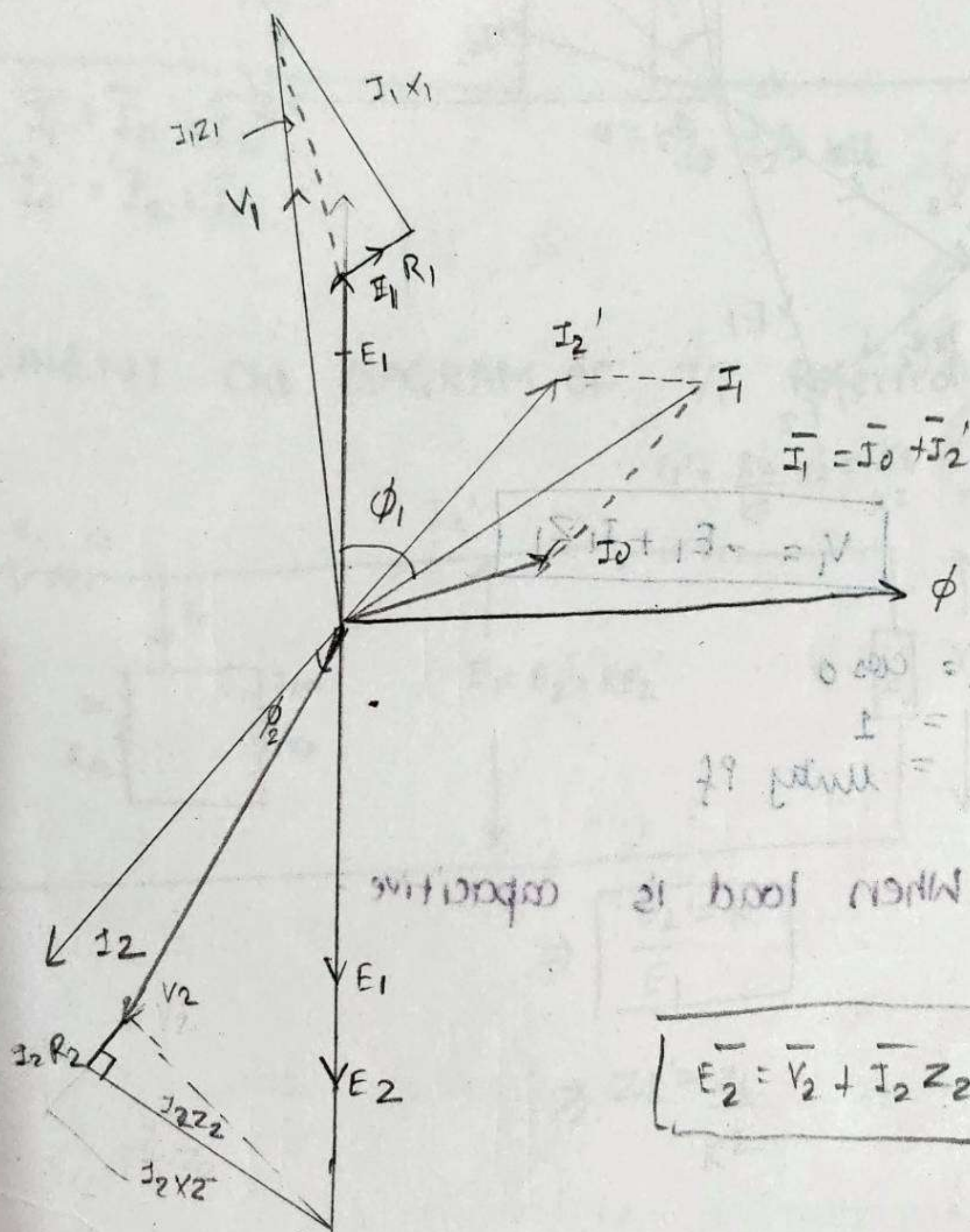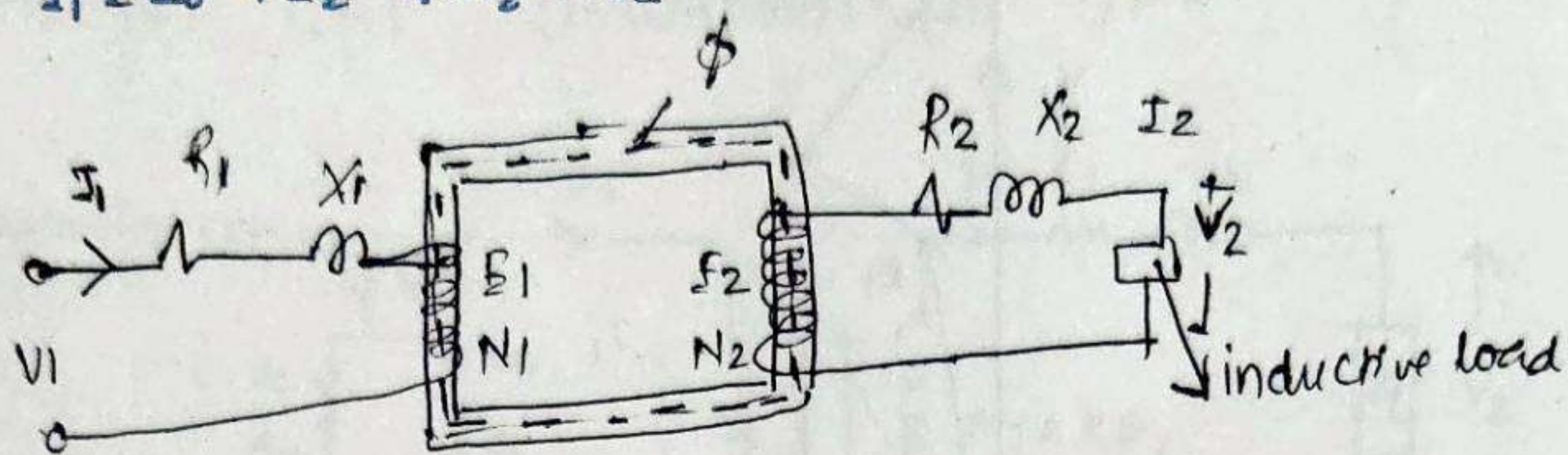- Load pf will be lagging i.e. I_2 will lag V_2
- $\bar{I}_1 = \bar{I}_0 + \bar{I}_2' \Rightarrow I_2' = KI_2$



$$\boxed{E_2 = V_2 + I_2 Z_2}$$

$$\bar{V}_1 = -\bar{E}_1 + \bar{I}_1 R_1 + j \bar{I}_1 X_1$$


$$V_1 = -E_1 + I_1 (R_1 + jX_1)$$

$$\boxed{V_1 = -E_1 + I_1 Z_1}$$

$$\boxed{V_1 - I_1 Z_1 = -E_1}$$

Case (ii) When load is resistive -

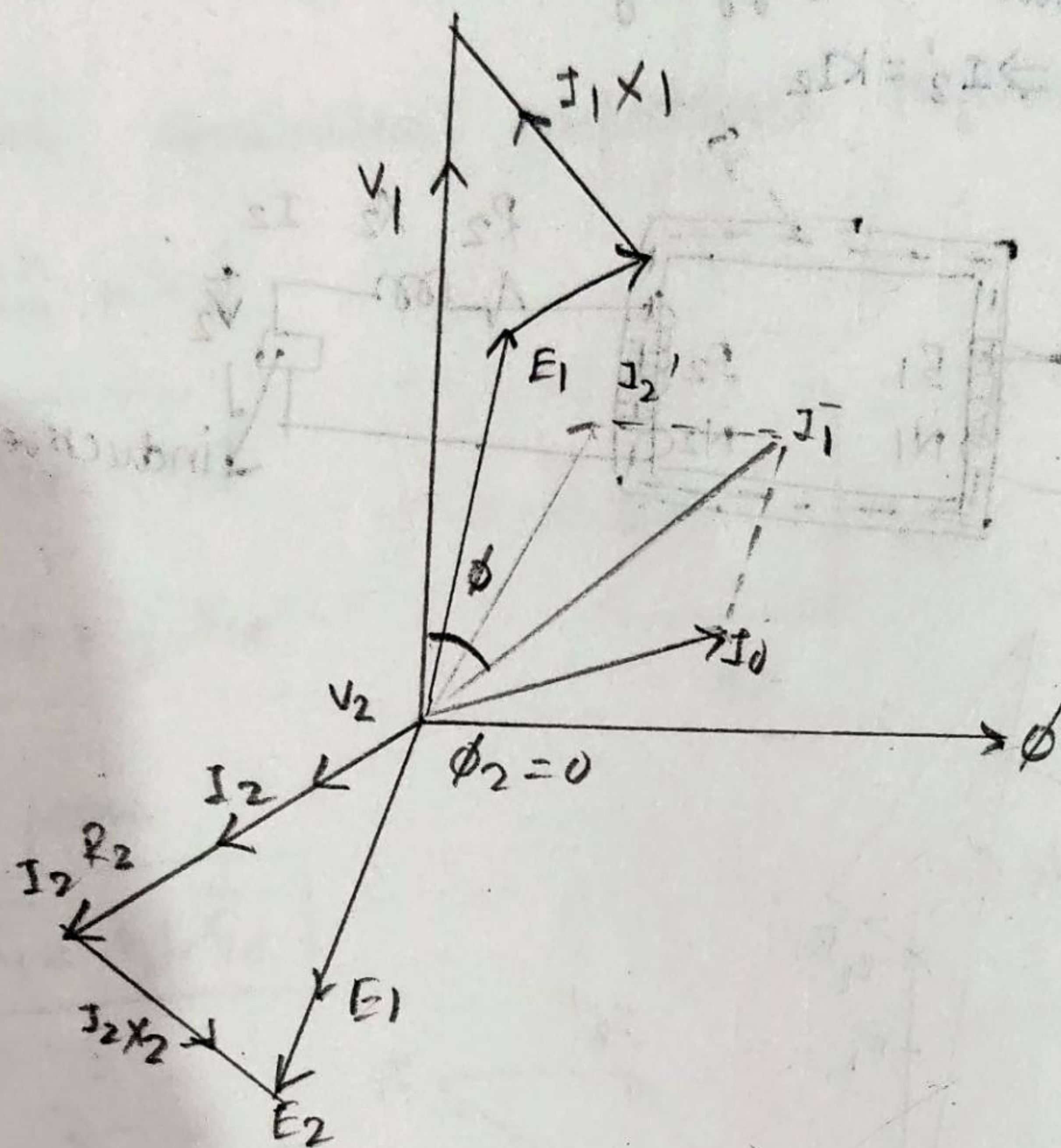
Here $I_2 \Delta V_2$ will be in same phase.





$$V_1 = -E_1 + I_1 Z_1$$

$$\begin{aligned} \cos \phi_2 &= \cos 0 \\ &= 1 \\ &= \text{Unity Pf} \end{aligned}$$


* EQUIVALENT CKT DIAGRAM OF T/F -

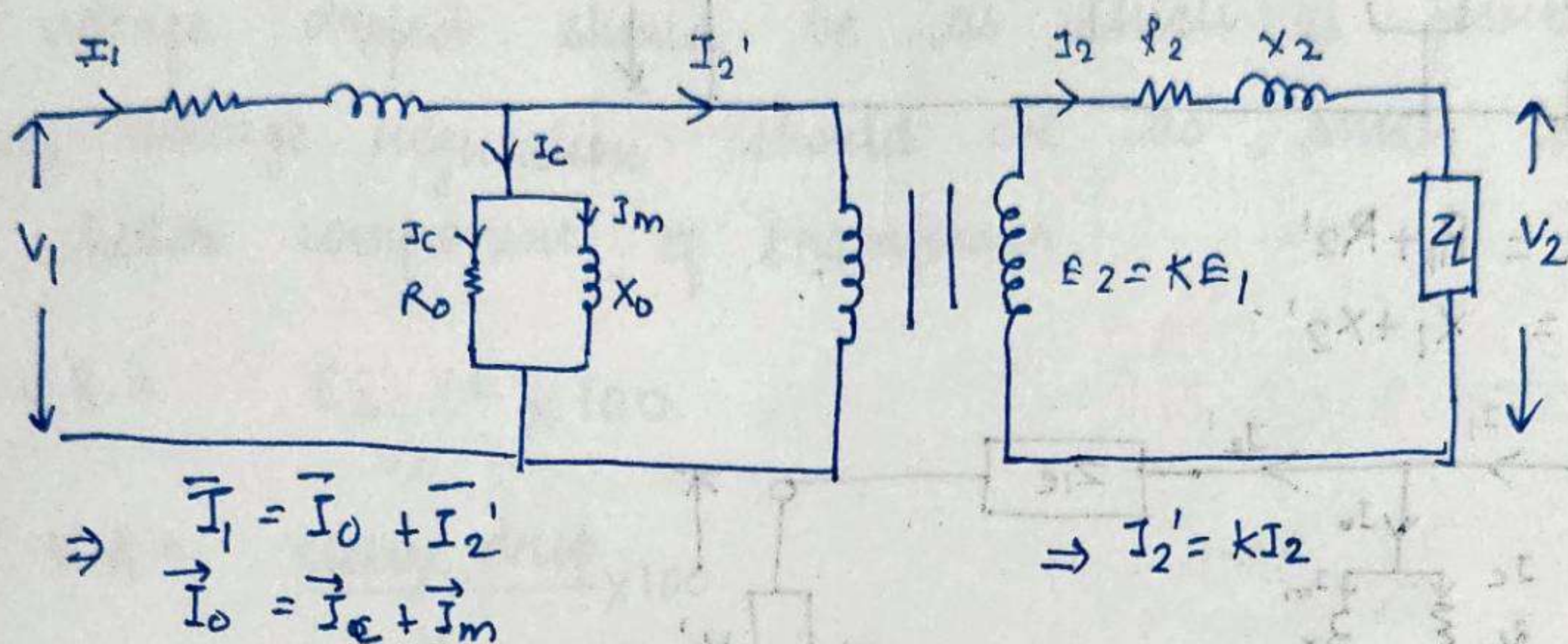

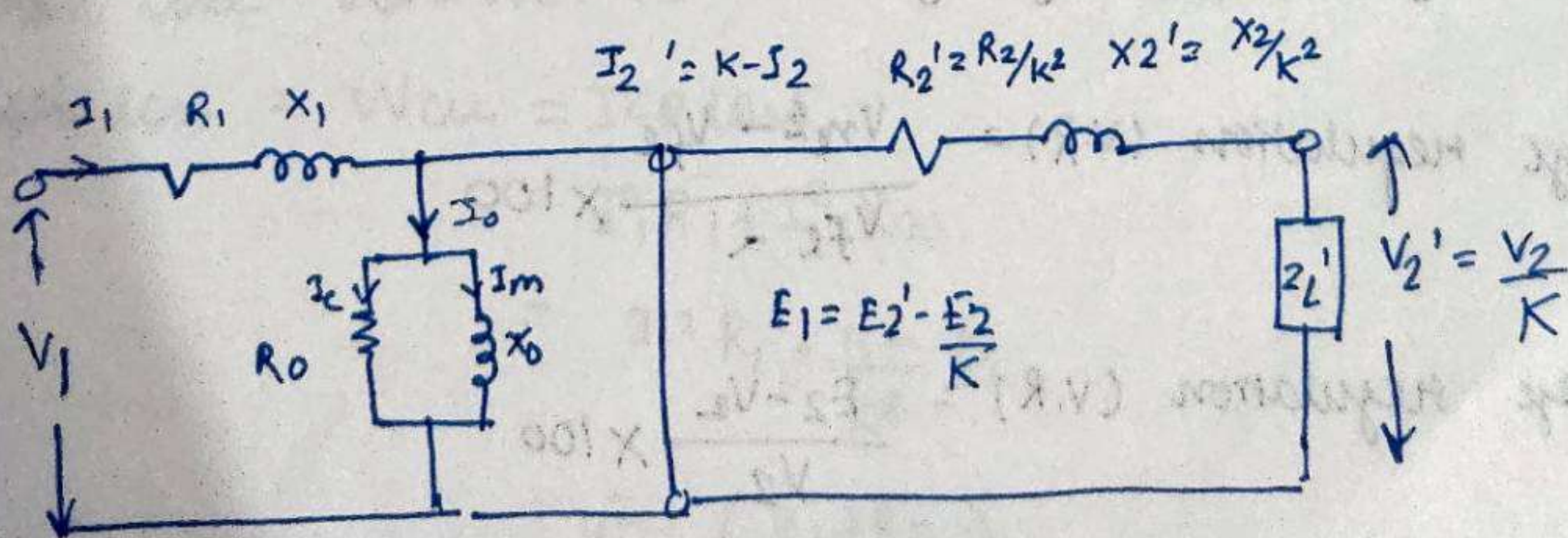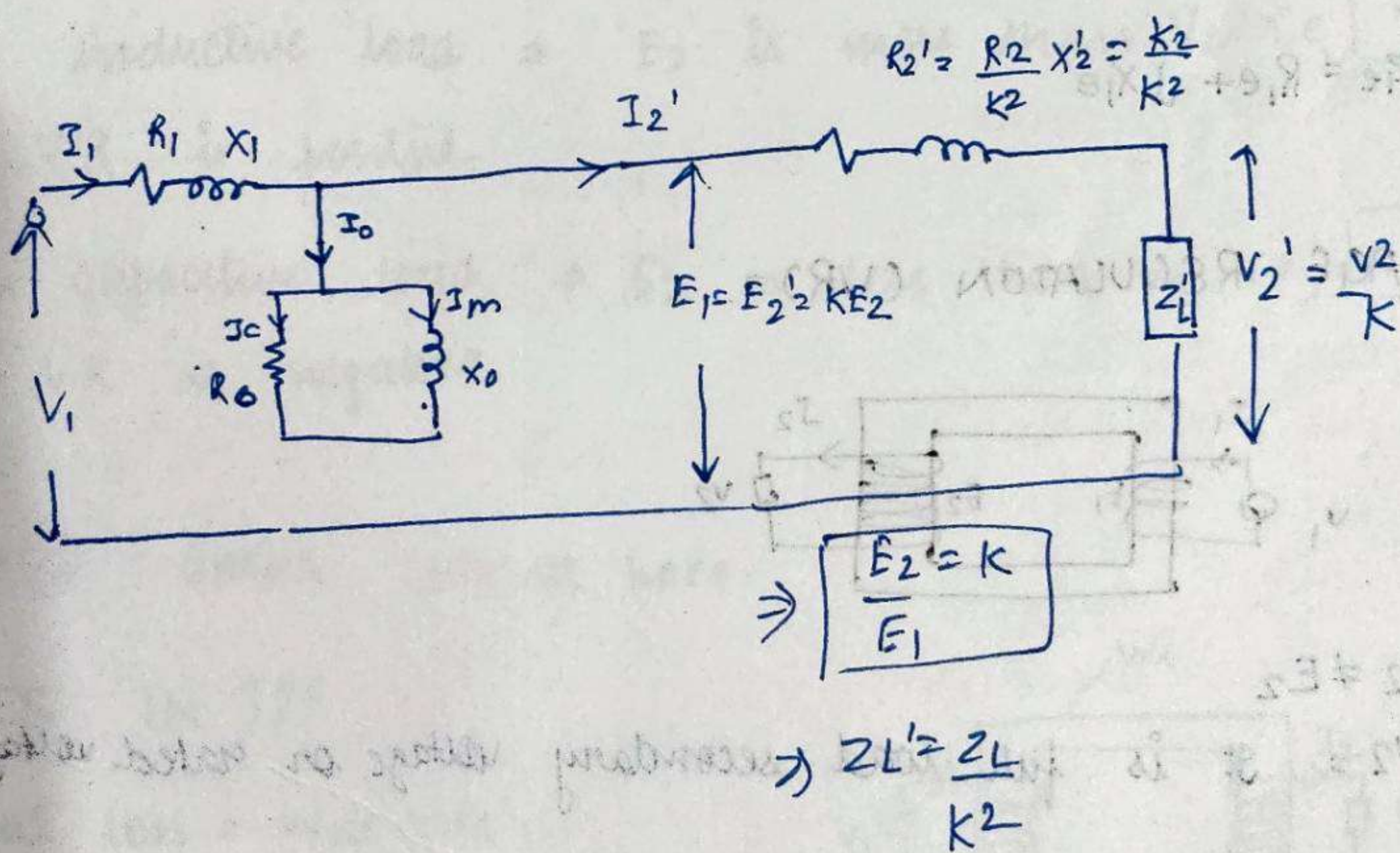* EQUIVALENT CKT DIAGRAM OF T/F Referred Primary side




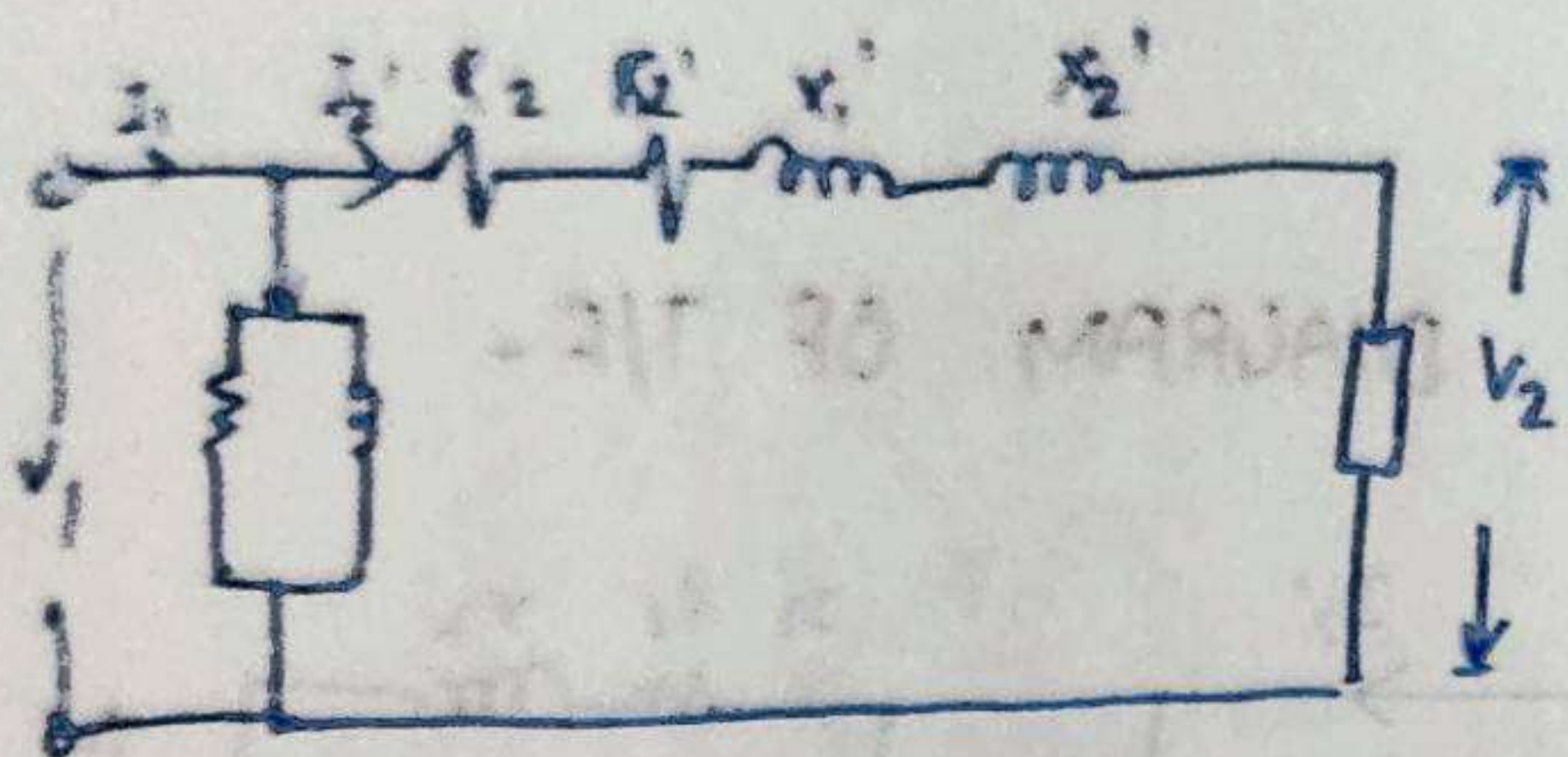* APPROXIMATE EQUIVALENT CIRCUIT OF T/F -




$$\Rightarrow R_{ie} = R_1 + R_2'$$

$$\Rightarrow X_{ie} = X_1 + X_2'$$

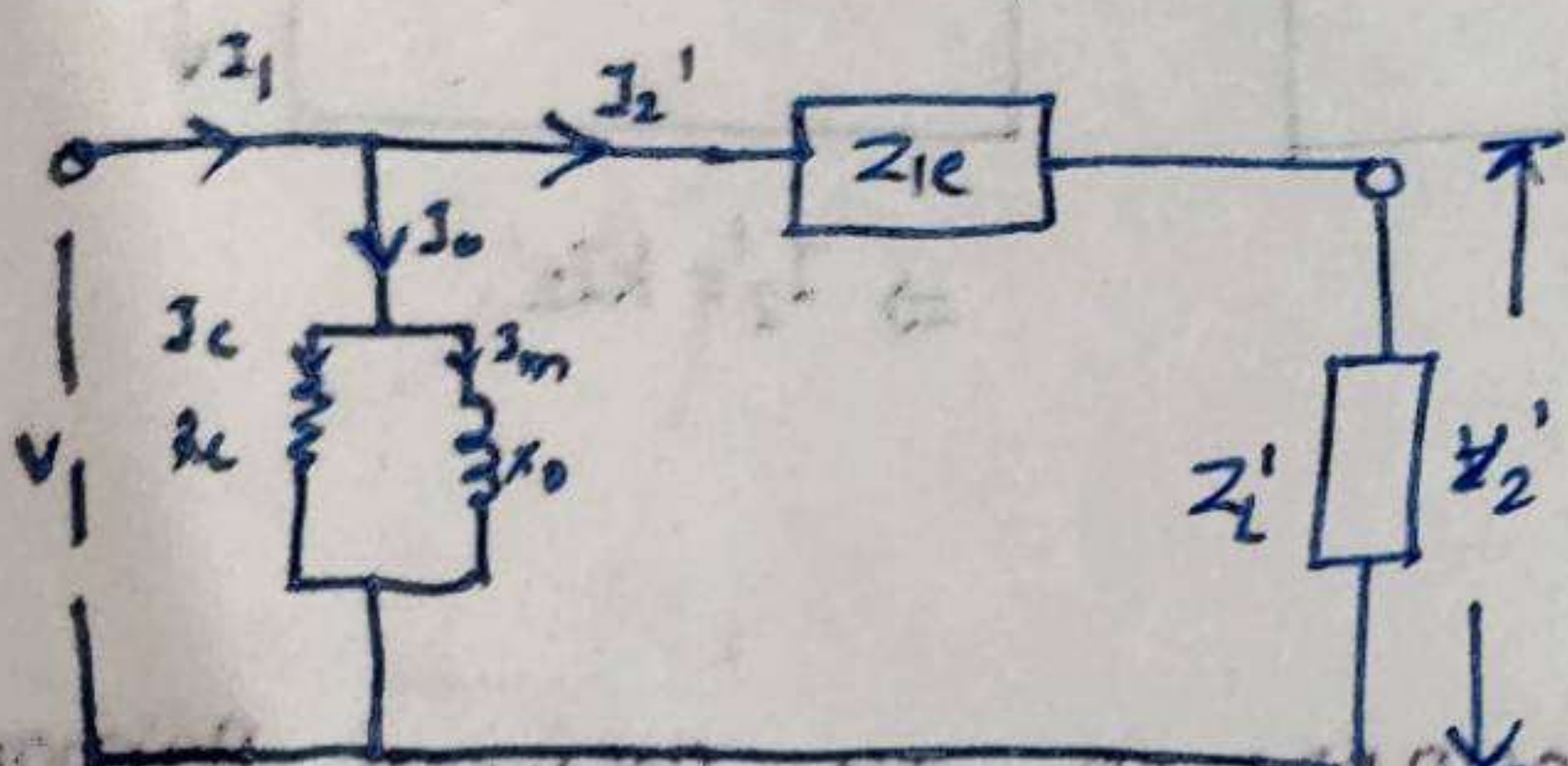

$$\Rightarrow Z_{ie} = R_{ie} + jX_{ie}$$

* VOLTAGE REGULATION (VR) -

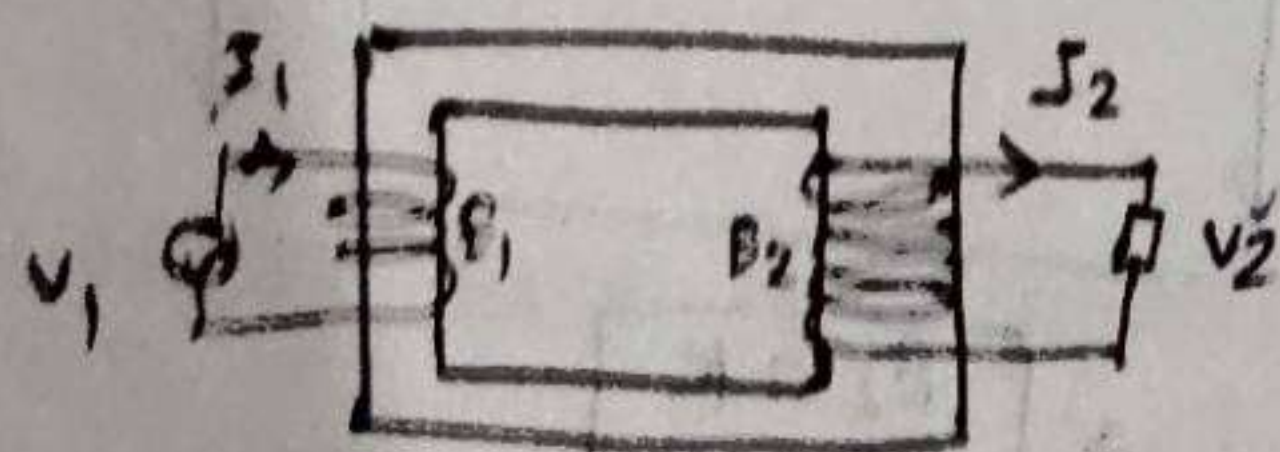

$$\Rightarrow V_2 \neq E_2$$

$\Rightarrow V_2$ is full load secondary voltage or rated voltage

$\rightarrow$ Percentage regulation / Voltage regulation -

$$\% \text{ Voltage regulation (VR)} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$

$$\% \text{ Voltage regulation (VR)} = \frac{E_2 - V_2}{V_2} \times 100$$

Definition-

The regulation is the change of V_2 when the full load is reduced to no-load.

Note-

- The voltage dropped should be as small as possible
- Hence, voltage regulation should be as small as possible for better component of transformer.
- $\% V.R = \frac{E_2 - V_2}{V_2} \times 100$
- $\% V.R = \frac{\text{Voltage drop}}{V_2} \times 100$
- VR also depends upon the Pf of load.
- For inductive load $\Rightarrow E_2$ is more than V_2 i.e., $E_2 > V_2$
- $\therefore \% V.R$ is positive
- For capacitive load $\Rightarrow E_2$ is less than V_2 i.e., $E_2 < V_2$
- $\therefore \% V.R$ is negative

Pg no-22 WORKS continue here-

* LOSSES IN T/F

$$\text{Total loss} = W_{cu} + W_i$$

$$\text{iron loss} = W_i = W_e + W_h$$

$$\text{copper loss} = W_{cu} = I^2 R_{\text{loss}}$$


$$= I_1^2 R_1 + I_2^2 R_2$$

$$= I_1^2 R_1 + \frac{I_1^2}{k^2} R_2$$

$$W_{cu} = I_1^2 \left(\frac{R_1 + \frac{R_2}{k^2}}{k^2} \right)$$

$$= I_1^2 (R_1 + R_2')$$

$$\therefore R_2' = \frac{R_2}{k^2}$$

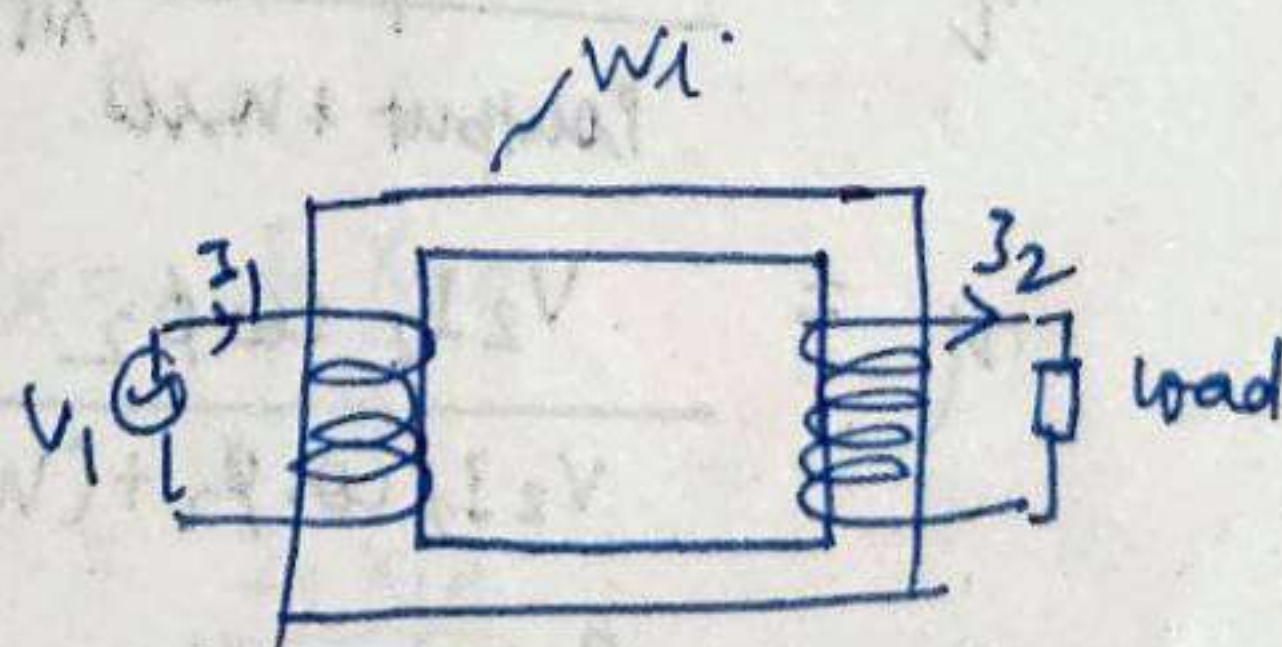

$$\frac{E_2}{E_1} = \frac{I_1}{I_2} = k$$

$$I_1 = k I_2$$

$$I_2 = \frac{I_1}{k}$$

similarly we can write



$$W_{cu} = I_1^2 \cdot R_{1e}$$

$$\therefore R_{1e} = R_1 + R_2'$$

$$W_{cu} = I_2^2 R_{2e}$$

$$R_{2e} = R_2 + R_1'$$

$$R_1' = k \cdot R_1$$

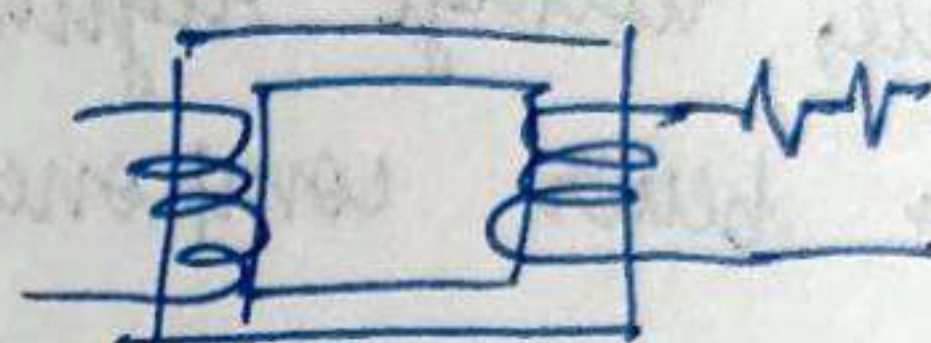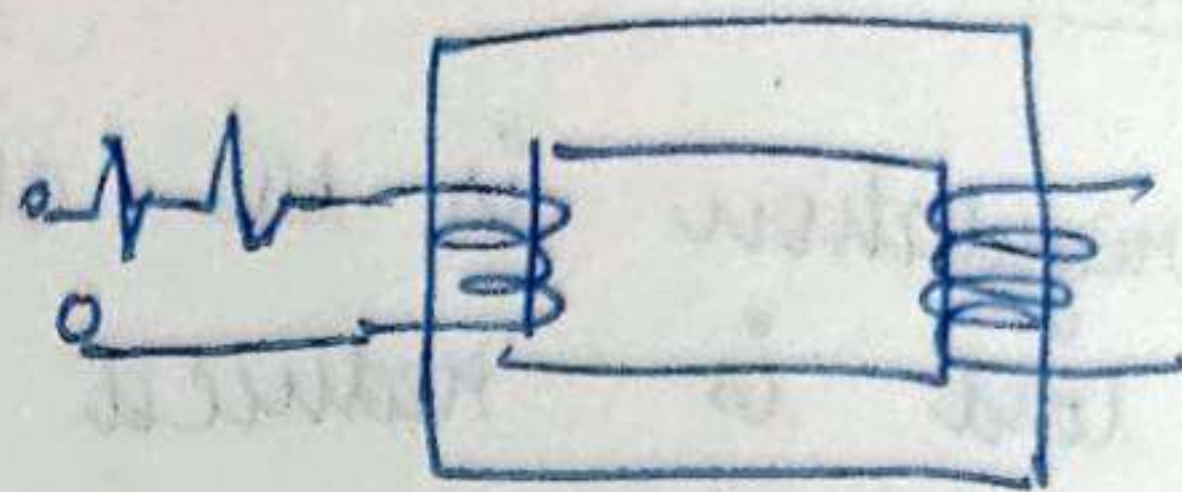

* EFFICIENCY OF T/F -

$$\eta = \frac{\text{O/P Power}}{\text{I/P Power}} \times 100$$

$$= \frac{P_{O/P}}{P_{I/P}} \times 100$$

$$= \frac{P_{O/P}}{P_{O/P} + \text{losses}} \times 100$$

$$\Rightarrow P_{O/P} = V_2 I_2 \cos \phi_2$$

$$W_{cu} = I_2^2 R_{2e}$$

$$W_i = W_e + W_h$$

$$\text{Total loss} = W_{cu} + W_i$$

$$\eta = \frac{P_{\text{output}}}{P_{\text{output}} + \text{losses}} \times 100$$

$$\eta = \frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + (W_i + W_{cu})} \times 100$$

$$V_2 = \text{Rated voltage} = V$$

$$I_2 = \text{Rated current} = I$$

$$\cos \phi_2 = \text{load P.f} = \cos \phi$$

$$\eta = \frac{VI \cos \phi}{VI \cos \phi + W_i + W_{cu}} \times 100$$

(or fractional load)



We know that load $\propto I^2$, so, efficiency of diff. load will be diff

Let, $x = \frac{\text{actual load}}{\text{full load}}$

$$\eta_x = \frac{x(VI \cos \phi)}{x(VI \cos \phi) + W_i + x^2 W_{cu}}$$

x is fraction of load
efficiency of fraction of load -

$$\therefore W_{cu} \propto I^2$$

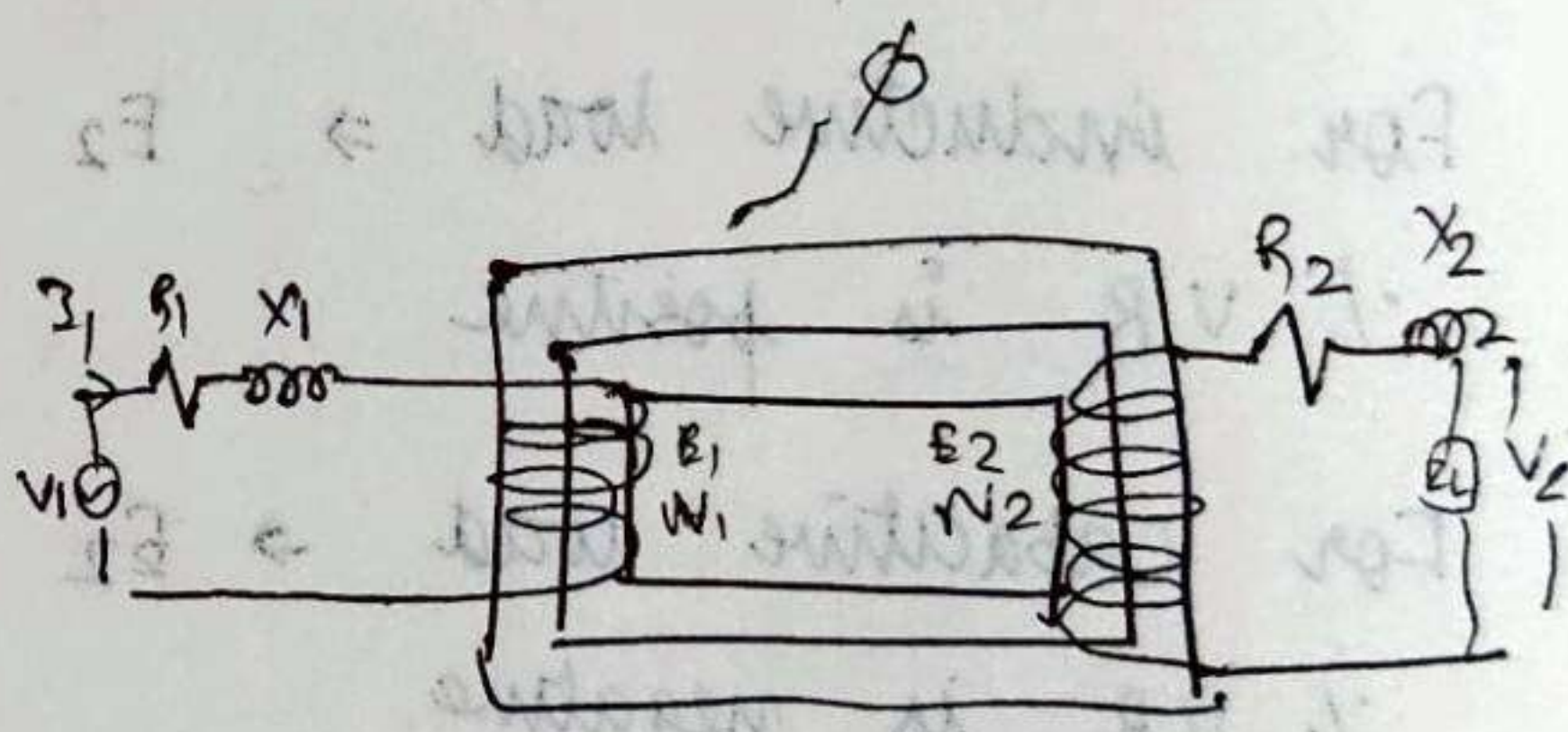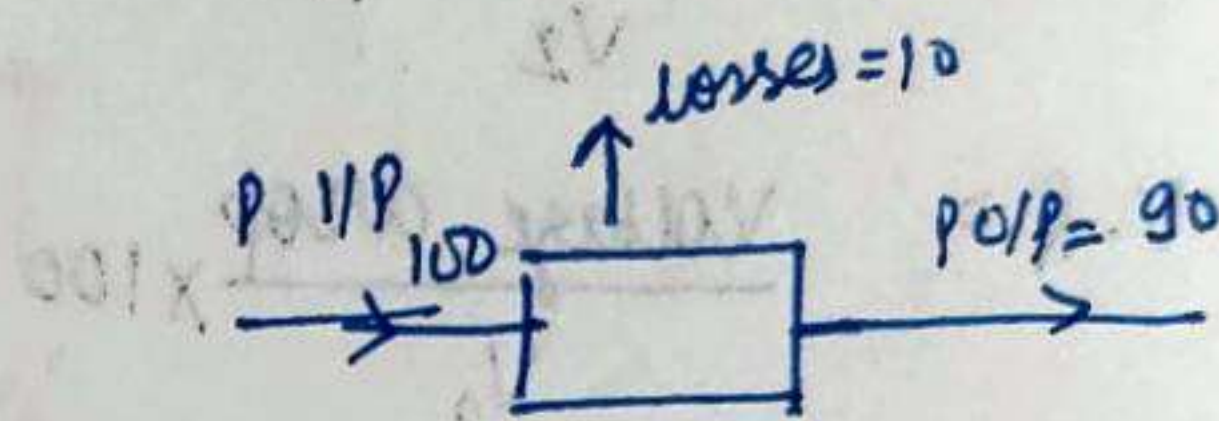

Formula -

$$\text{Voltage drop} = I_2 R_{2e} \cos \phi \pm I_2 X_{2e} \sin \phi$$

$$R_{2e} = k^2 R_1 + R_2$$

$$R_{2e} = k^2 R_1 + R_2$$

$$X_{2e} = X_1' + X_2$$

$$= k^2 X_1 + X_2$$

- Take (+) sign of load lagging
- Take -ve sign if load is leading

$$\begin{aligned} \% VR &= \frac{\text{Voltage drop}}{V_2} \times 100 \\ &= \frac{I_2 R_{2e} \cos \phi \pm I_2 X_{2e} \sin \phi}{V_2} \times 100 \end{aligned}$$

$$\% VR = \frac{I_1 R_{1e} \cos \phi \pm I_1 X_{1e} \sin \phi}{V_1} \times 100$$

* Constants of transformers-

$$\begin{aligned} (1) \text{ Per unit resistance drop} &= V_R \Rightarrow \frac{I_2 R_{2e}}{E_2} \\ &\Rightarrow \frac{I_1 R_{1e}}{E_1} \end{aligned}$$



$$\begin{aligned} (2) \text{ Per unit reactance drop} &= V_X = \frac{I_2 X_{2e}}{E_2} \\ &= \frac{I_1 X_{1e}}{E_1} \end{aligned}$$



* LOSSES IN T/F-

$$(1) \text{ Iron loss - core loss - } W_i \Rightarrow W_i = W_e + W_h$$

$$\rightarrow W_e \propto B_m^2 f^2$$

$$B_m \propto \phi_m$$

$$\rightarrow W_e \propto \phi_m^2 f^2$$

eddy current loss.

hysteresis loss

$$W_e = \eta B_m^2 f^2 (\text{volume})$$

$\Rightarrow \eta \text{ const.}$

$B_m \Rightarrow \text{max flux density.}$

$$B_m = \frac{\phi_m}{A} \text{ Wb/m}^2$$

$\rightarrow V \propto \phi m f$
 $\rightarrow W_h = \eta B_m^{1.6} f$ (volume)
 $\rightarrow W_h = B_m^{1.6} S$

high load $\rightarrow$ low resistance
 $\therefore P \propto \frac{1}{R}$
 less load $\rightarrow$ more resistance.
 $R \propto \frac{1}{I}$ & $P \propto I$
 More watt $\rightarrow$ more load $\rightarrow$ low R.

$\rightarrow$ So eddy current loss depends upon $\rightarrow W_e \propto B_m^2 f^2$
 $\rightarrow$ & hysteresis loss depend upon $\rightarrow W_h \propto B_m^{1.6} f$

For practical purpose -



* $W_e \propto B_m^2 f^2$
 * $W_h \propto B_m^{1.6} f$ (approx)

(2) Copper loss - variable loss

$W_{cu} = I^2 R$
 $W_{cu} \propto I^2$
 $W_{cu} \propto (\text{current})^2$ ($\because I \propto \text{load}$)

Note -

1 unit = 1 kWh = 1 unit of electricity

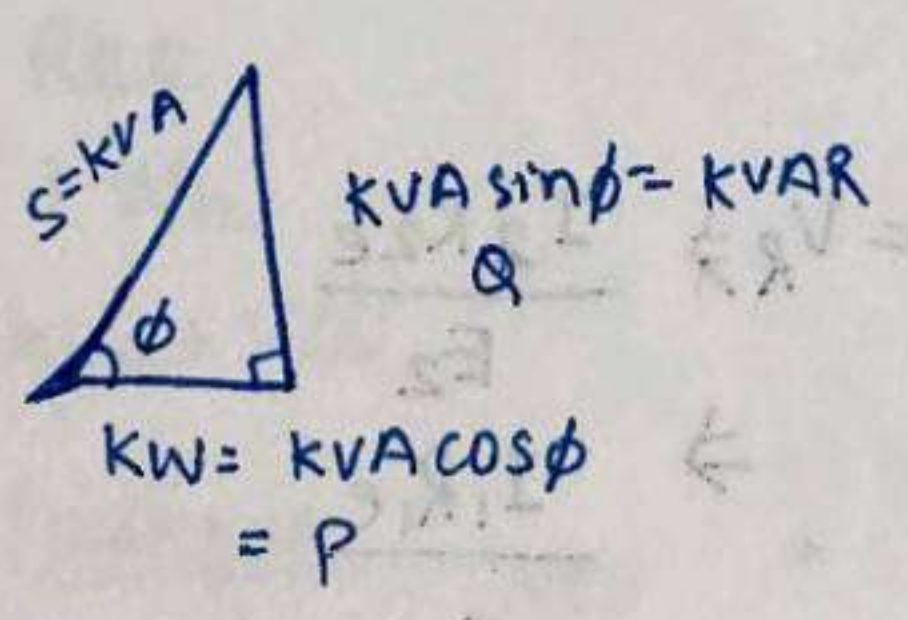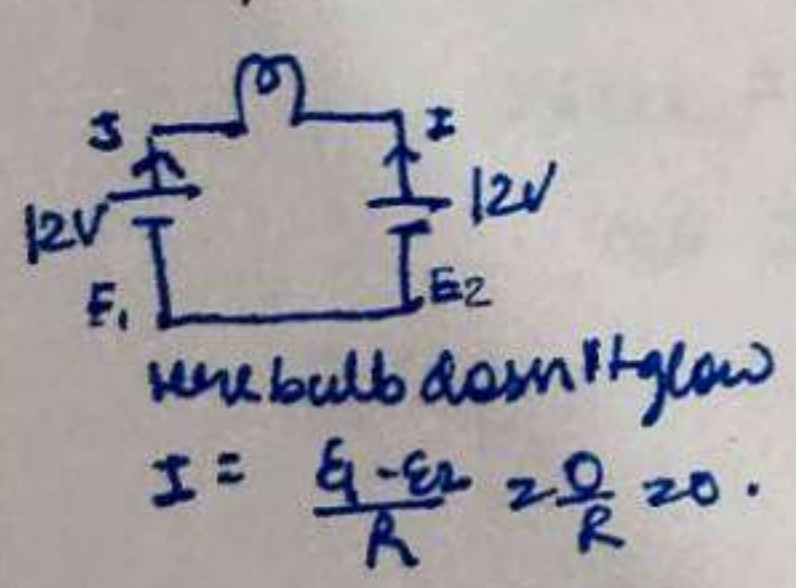


Iron loss doesn't depend upon load
 that's why it's also called fixed load or constant loss.
 Cu loss is variable loss.

disadvantage $\rightarrow$ SC & OC

Short ckt -

Suppose -

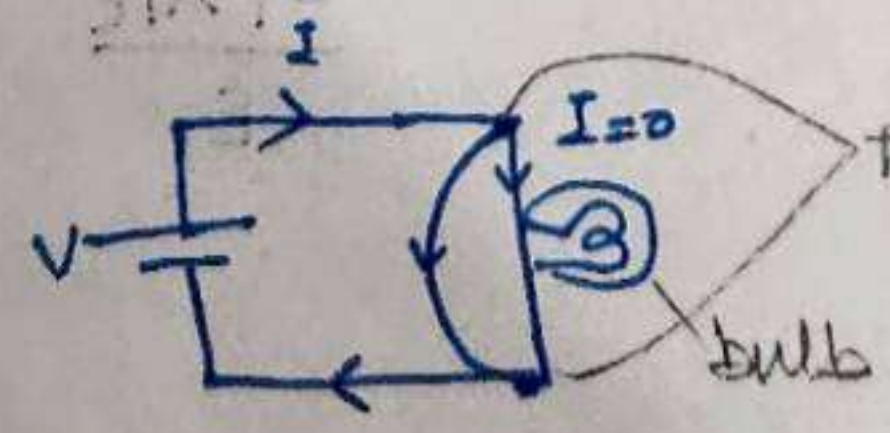

These 2 terminals attached to itself
 Current - high to low

No resistance $\therefore I \propto \frac{1}{R} = I \propto \frac{1}{0} = I = \infty$

i.e., when no resistance is present, current is more & heat is more
 that's why SC is happen & sometimes fire is also caused

Open ckt -

When ckt is open then no current will flow
 $R \propto \frac{1}{I}$ $\therefore R \propto \frac{1}{0} = R = \infty$

infinite Resistance.

* Maximum efficiency of T/F -

$$\eta_x = \frac{x(VA \cos \phi)}{x(VA \cos \phi) + W_i + x^2 W_{cu}}$$

divide above eqn by x , then we get -

$$\eta_x = \frac{VA \cos \phi}{VA \cos \phi + \frac{W_i}{x} + x \cdot W_{cu}}$$

→ For η_x to be max, the denominator must be minimum.

→ For min and max value $\frac{d}{dx} (VA \cos \phi + \frac{W_i}{x} + x W_{cu}) = 0$.

$$\Rightarrow \frac{d}{dx} \left\{ (VA \cos \phi) + \frac{W_i}{x} + x W_{cu} \right\} = 0$$

$$\Rightarrow \frac{d}{dx} (VA \cos \phi) + \frac{d}{dx} \left(\frac{W_i}{x} \right) + \frac{d}{dx} (x W_{cu}) = 0$$

$$\Rightarrow 0 + (-x^{-2} \cdot W_i) + 1 \cdot W_{cu} = 0$$

$$\Rightarrow -\frac{W_i}{x^2} = -W_{cu}$$

$$\boxed{W_i = x^2 \cdot W_{cu}} \rightarrow \text{Variable or Cu loss.}$$

for fractional load - Iron loss or constant loss

$$\therefore \boxed{\text{Constant loss} = x^2 (\text{Variable loss})}$$

→ for full load, $x=1$ then $\boxed{W_i = W_{cu}}$

* ALL DAY EFFICIENCY OF T/F -

• The ratio of the total energy O/P to the total energy I/P is called all day efficiency of transformer.

$$\% \text{ All day } \eta = \frac{\text{O/P energy in kWh per day}}{\text{I/P energy in kWh per day}} \times 100$$

$$\boxed{1 \text{ unit} = 1 \text{ kWh.}}$$

• Distribution T/F are used for distributive & commercial loads. The loads on T/F varies considerably during a day.

- For most period of day the load of T/F is 30-40% of full load or even less than this.
- But primary wdgy remains energised at it's rated time for 24 hrs to provide continuous supply to consumer.
- The core loss depends upon voltage takes place continuously for all loads but cu loss depend upon loads.
- Hence, power efficiency can't give its true measure for a distribution T/F.
- Therefore, energy o/p is calculated in kwh. and various losses are calculated in kwh.

* TESTING OF TRANSFORMER-

(i) direct test on T/F

(ii) indirect test on T/F

→ No load test (open ckt test) → For iron loss (W_i) calculation

→ Short ckt test → For copper loss (W_{cu}) calculations.

(iii) polarity test

(iv) Back to back test → Sumpner's test


• DIRECT TEST ON T/F / LOAD TEST-

→ In this method load is directly connected to the T/F. A load is varying from no load to full load

→ This test is suitable for small transformers becoz large loads can't be

→ In this test there is large ^{no. of} power loss

Experimental Set-up - 10

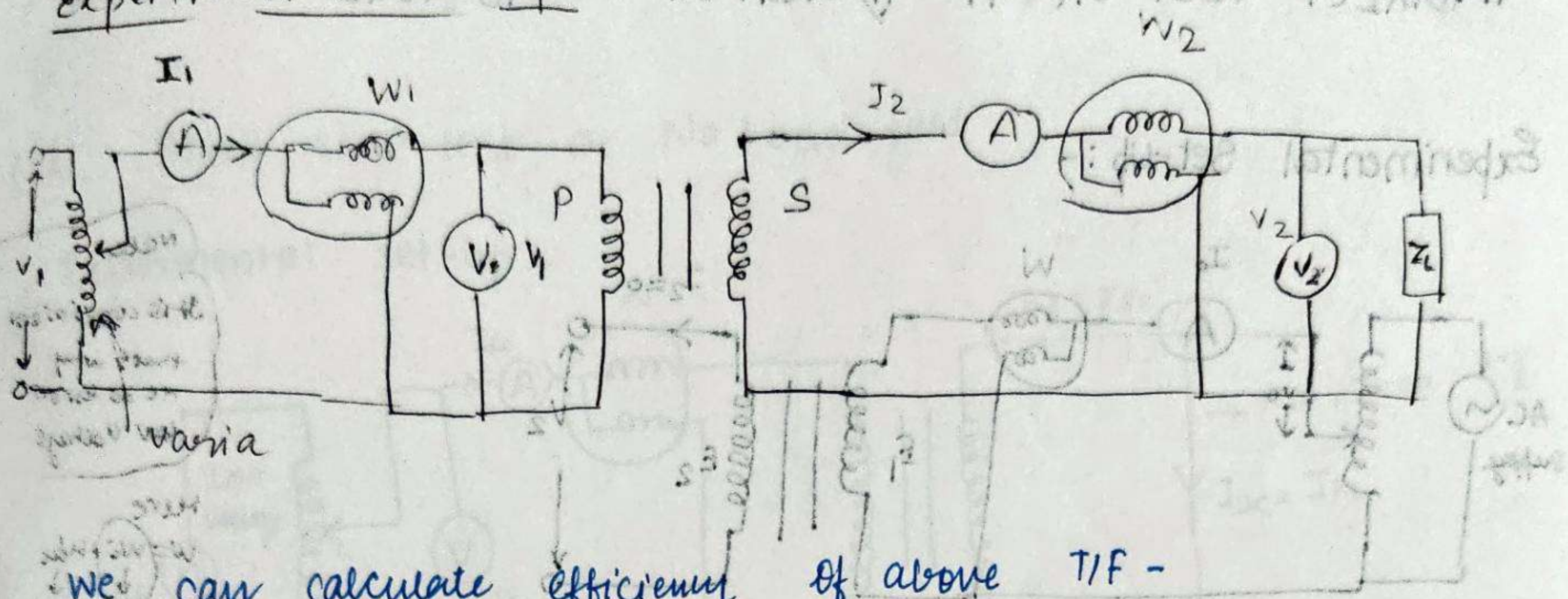


We can calculate efficiency of above T/F -

$$\% \eta = \frac{\text{O/P Power}}{\text{I/P Power}} \times 100$$

$$= \frac{W_2}{W_1} \times 100 \quad (\text{From fig.})$$

$$\text{Voltage regulation} = \% VR \Rightarrow \frac{E_2 - V_2}{V_2} \times 100$$


Graph - (efficiency)

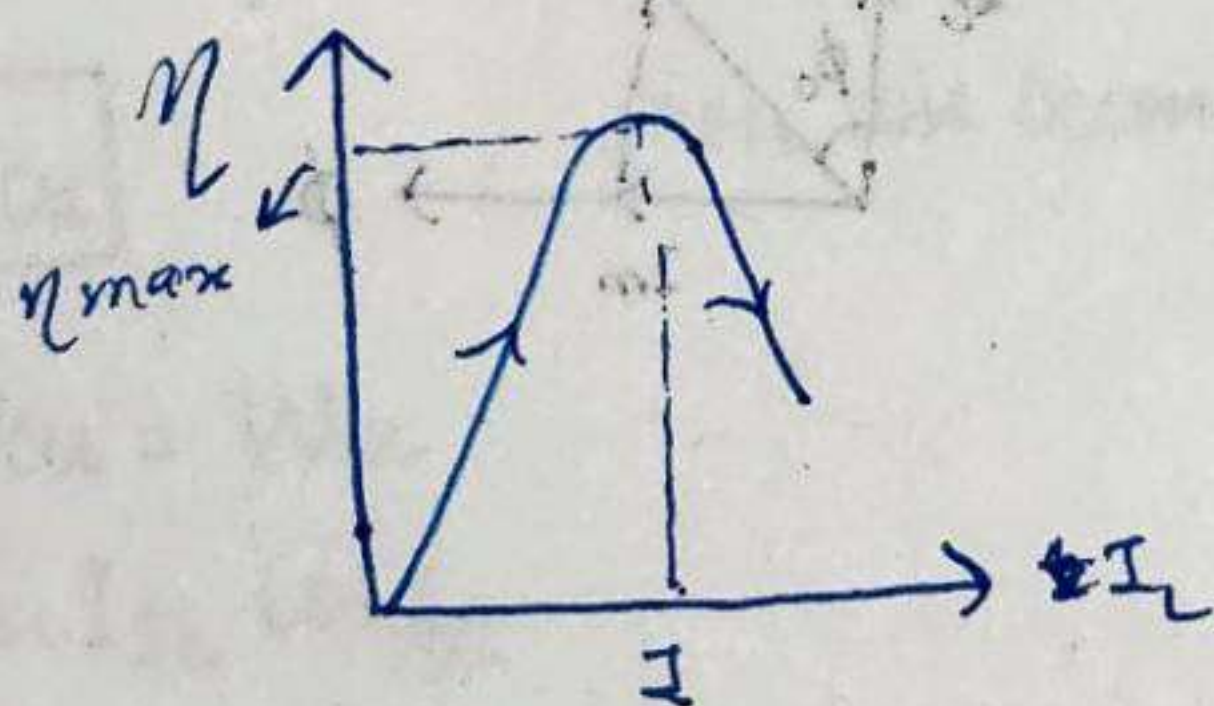

- With $\uparrow$ in load efficiency also $\uparrow$. At a certain load when, $W_{cu} = W_{ci}$ efficiency becomes maximum & thereafter again it's starts decreasing


- Regulation or V.R. also increases as load $\uparrow$.

Graph - (VR)

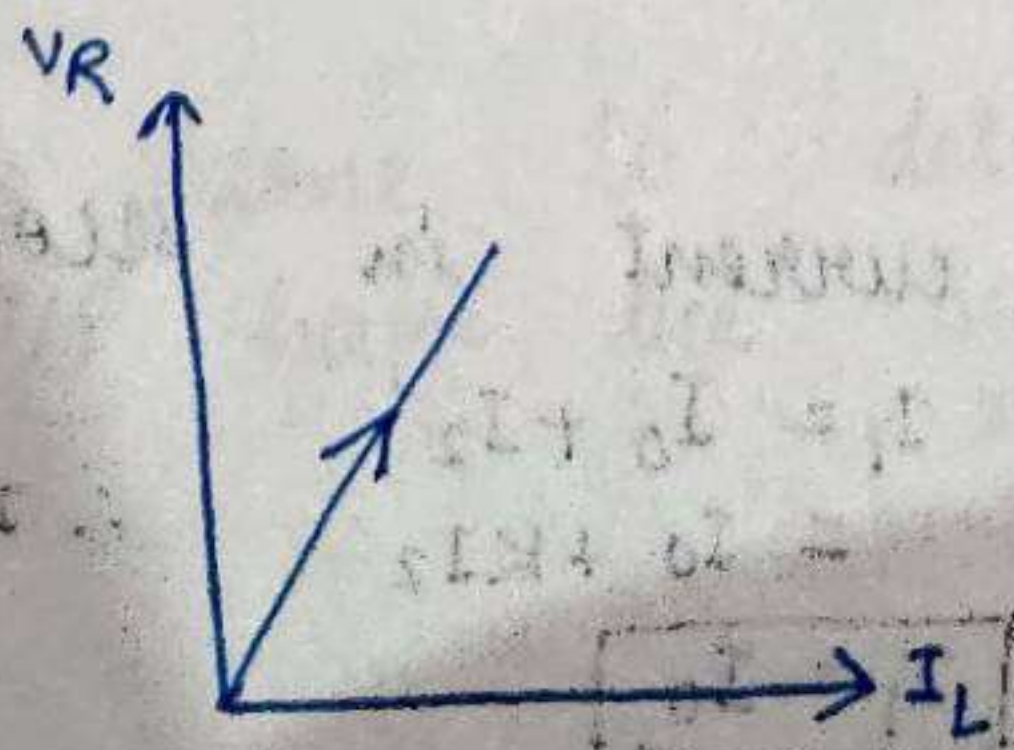

• INDIRECT TEST ON T/F - (i) OPEN CKT OR NO load Test -

Experimental Set-up :-

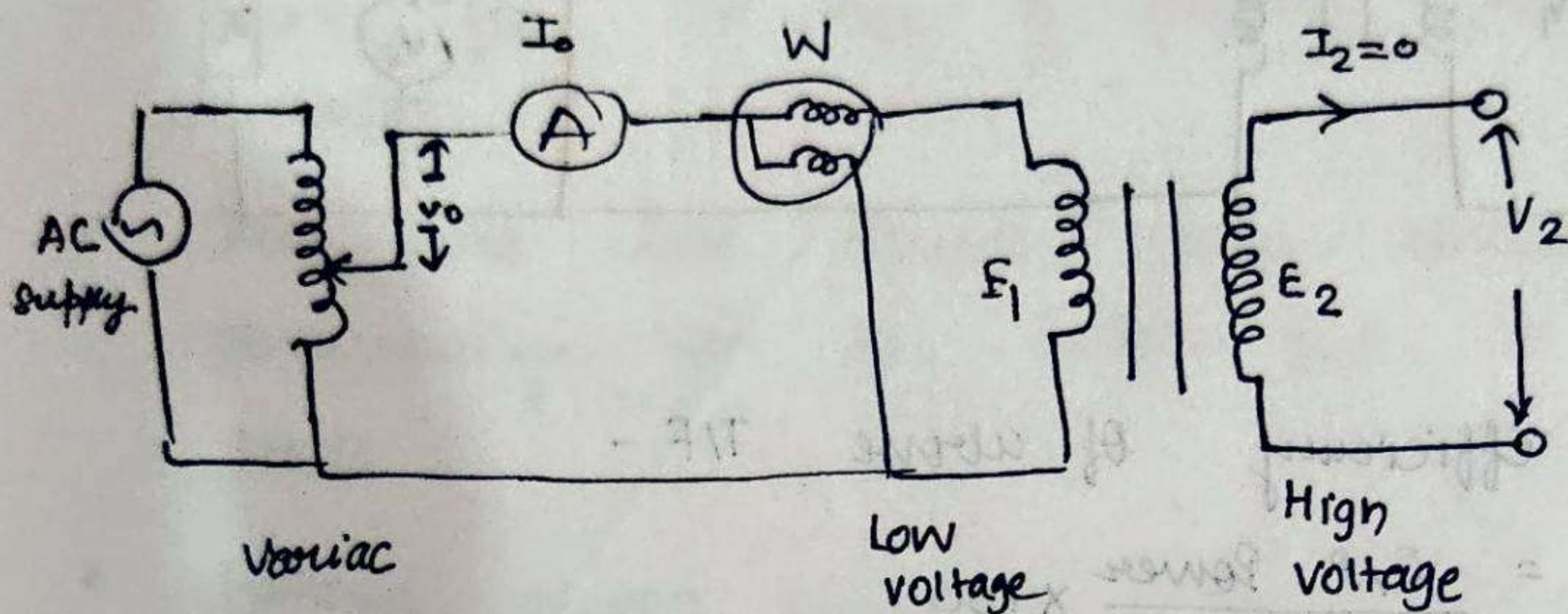

Note
It is convenient
that's why
we do test on
low voltage

Here
 $W = W_c + W_m$
↓
test

V_0 = rated voltage at no load

W_0 = I/p power

I_0 = I/p current at no load (3% to 5% of rated current)

$I_0 = I_c + I_m$

$I_0 = \sqrt{I_c^2 + I_m^2}$

$I_c = I_0 \cos \phi_0$

$I_m = I_0 \sin \phi_0$

$\cos \phi_0$ = no-load P-f



$W_0 = V_0 I_0 \cos \phi_0$

$\cos \phi_0 = \frac{W_0}{V_0 I_0}$

$\sin \phi_0 = \sqrt{1 - \cos^2 \phi_0}$

$R_0 = \frac{V_0}{I_c}$

$X_0 = \frac{V_0}{I_m}$
Reactance

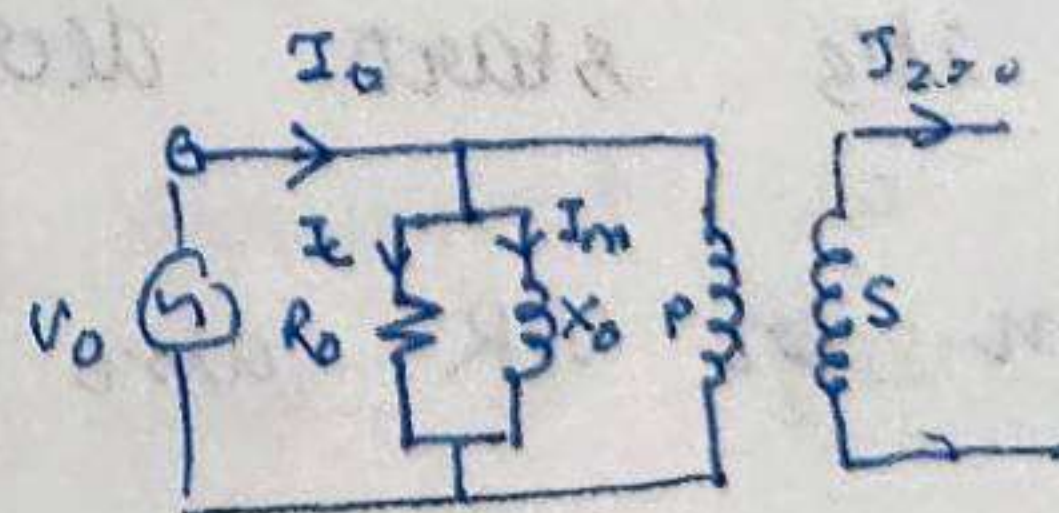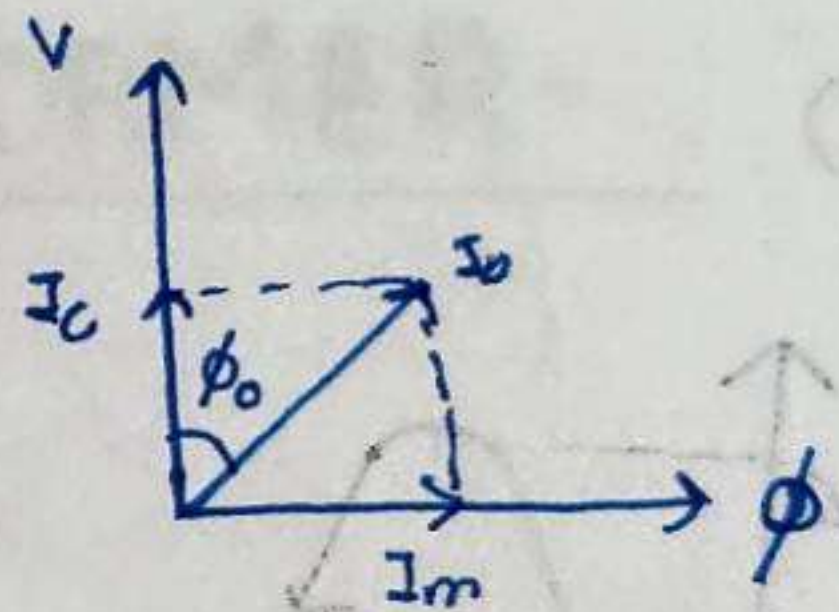


→ In open ckt test there is no current in secondary side
so I_2 is 0 and total current is $I_1 = I_0 + I_2$
 $= I_0 + 0$
 $\therefore I_1 = I_0$

→ so current drawn by primary $I_1 = I_0$ which is only 3 to 5% of the rated current, therefore Cu loss in case of no load will be negligible.

→ Therefore the only loss which is occurring in T/F is iron loss.

(ii) Short ckt-test or No load test

Experimental set-up:-

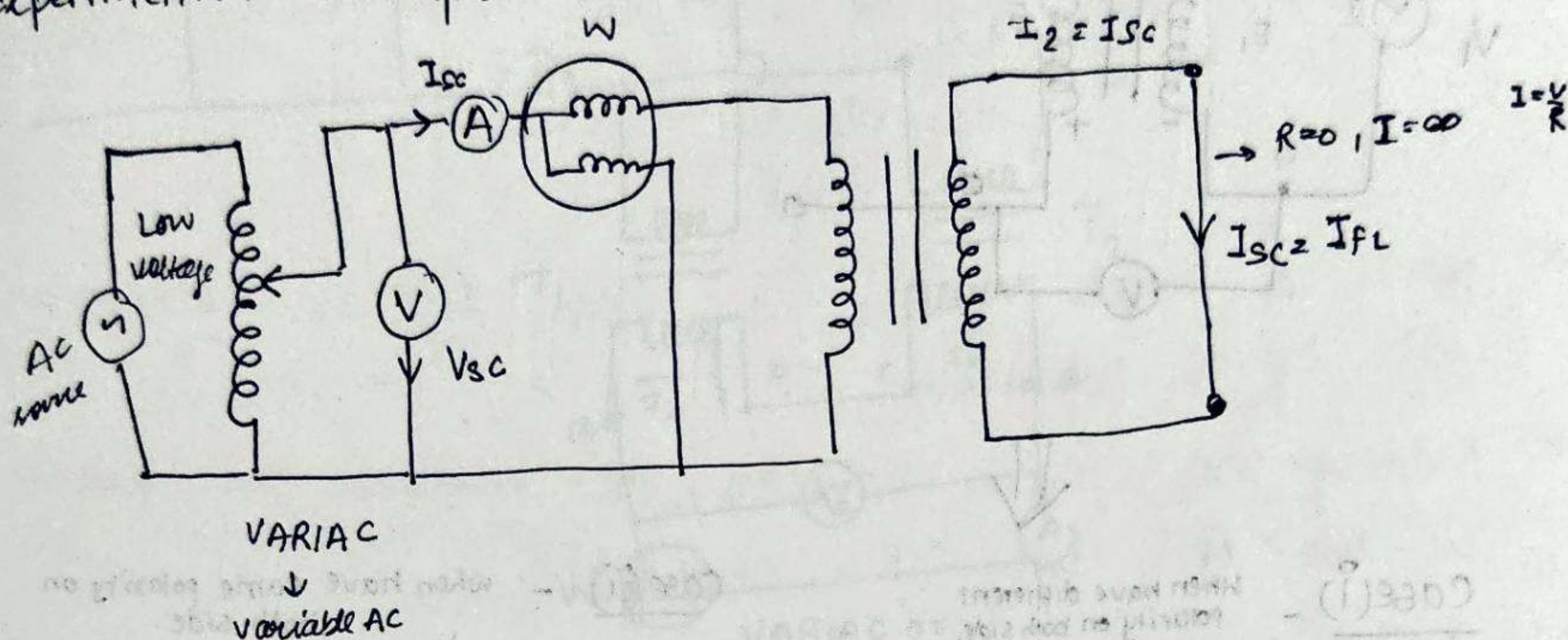

$$W = W_i + W_{cu}$$

$$W_i \propto V^2$$

$$W_{cu} \propto I_{FL}^2$$

At low voltage, iron loss becomes negligible as compared to Cu loss.

Here,

$$W = W_{cu}$$

iron loss becomes negligible i.e. 0.


$$W = W_{cu} = W_{sc}$$

$$W_{sc} = V_{sc} I_{sc} \cos \phi_{sc}$$

$$W_{sc} = I_{sc}^2 R_{ie}$$

$$R_{ie} = \frac{W_{sc}}{I_{sc}^2}$$
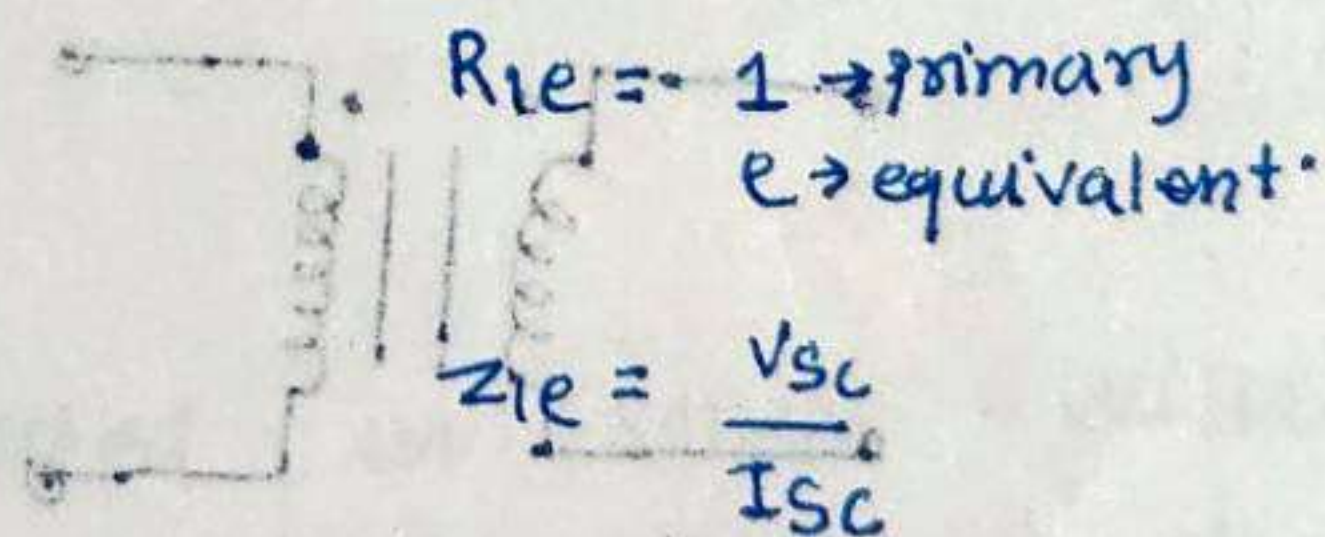
$$\therefore R_{ie} = R_1 + R'_2 \quad \& \quad R'_2 = R_2 / K^2$$




$$Z_{ie} = \sqrt{R_{ie}^2 + X_{ie}^2}$$


© POLARITY TEST-

→ This test is done to determine which ends of two winding of T/F have the same polarity at same time.

→ Ckt diagram -

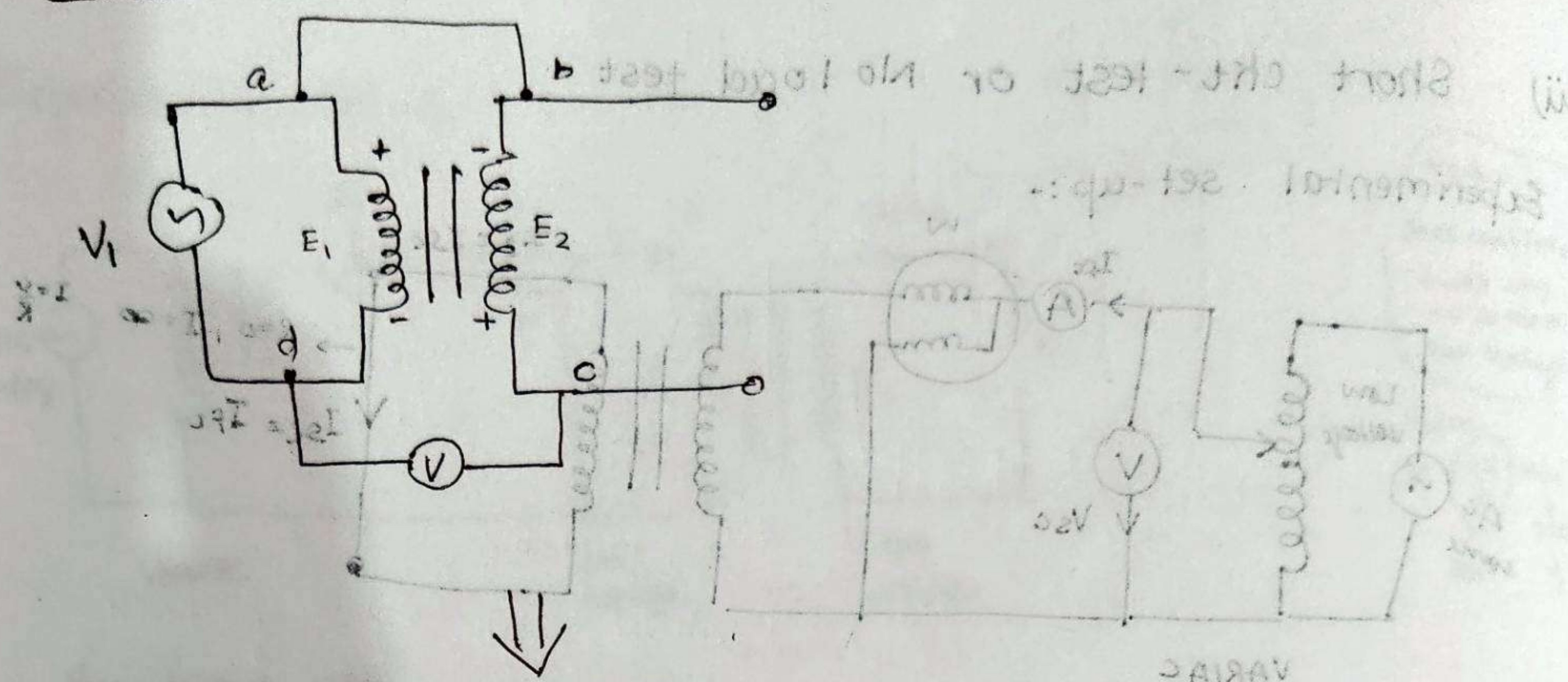


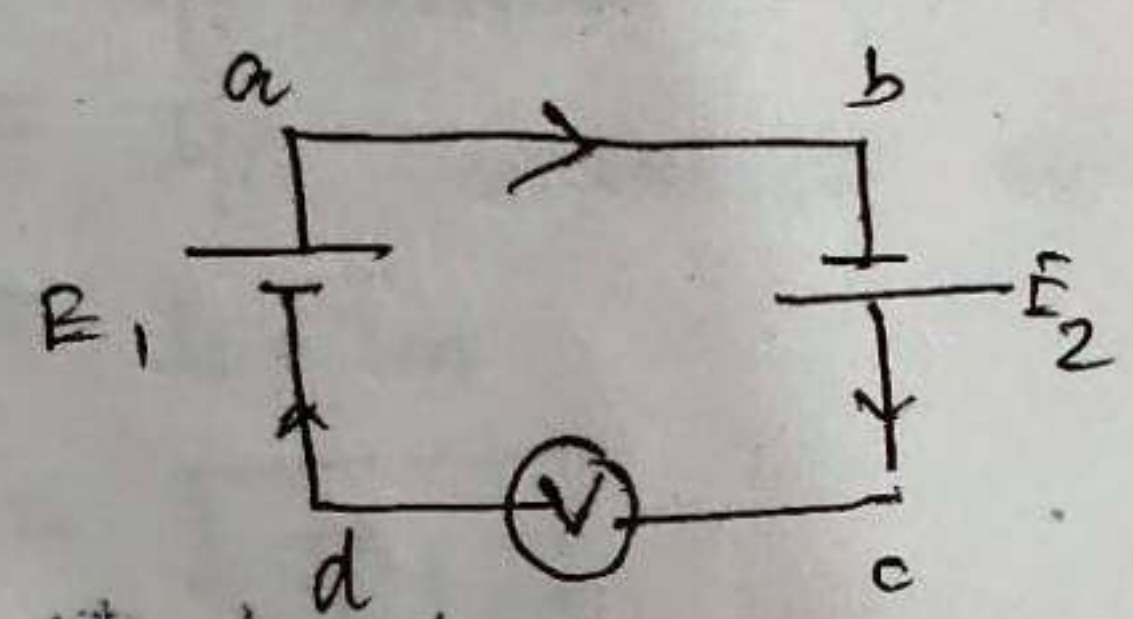Case (i) - When have different polarity on both side.




Net voltage = Sum of the two voltages
 $= (E_1 + E_2)$

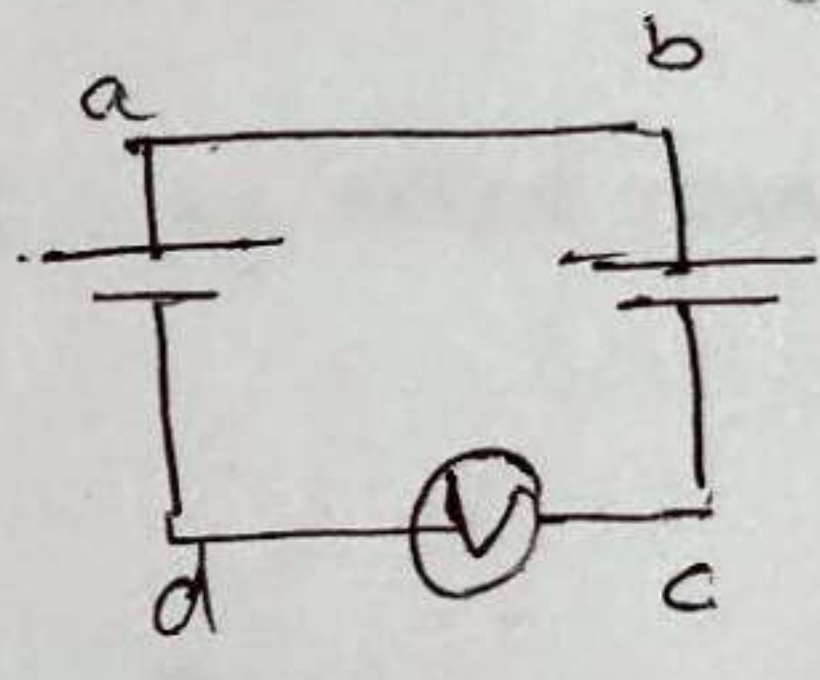Case (ii) - when have same polarity on both side.




Net voltage = $E_1 - E_2$

→ Symbol for Same polarity -

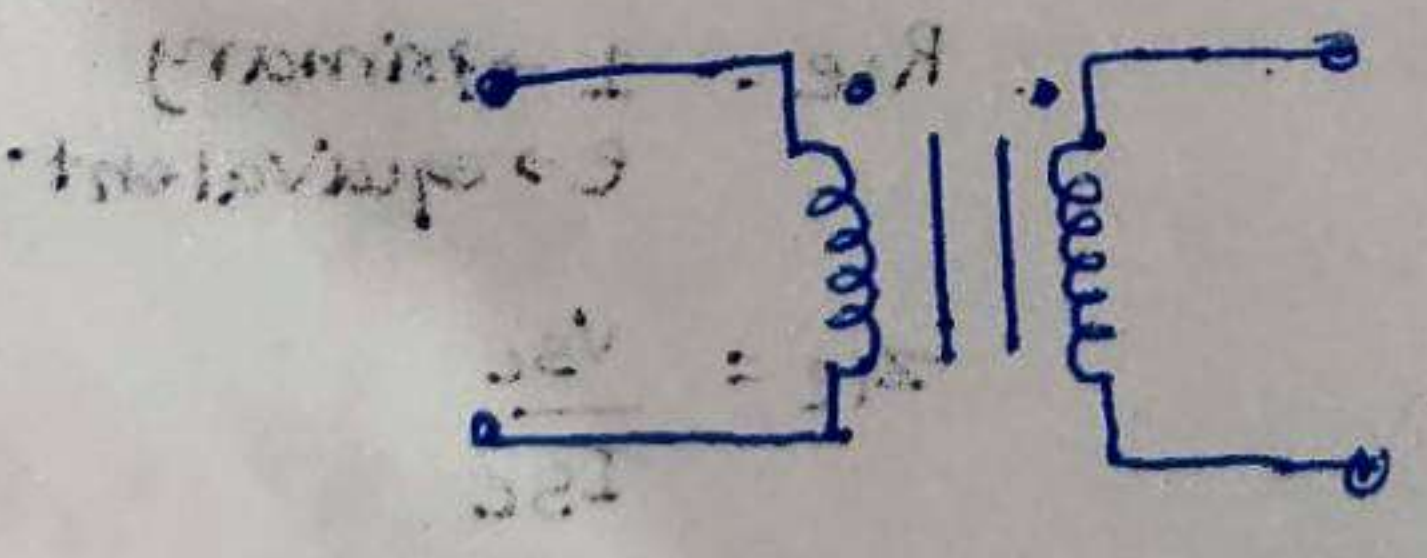


⑥. SUMPNE'S TEST (Back to back test):-

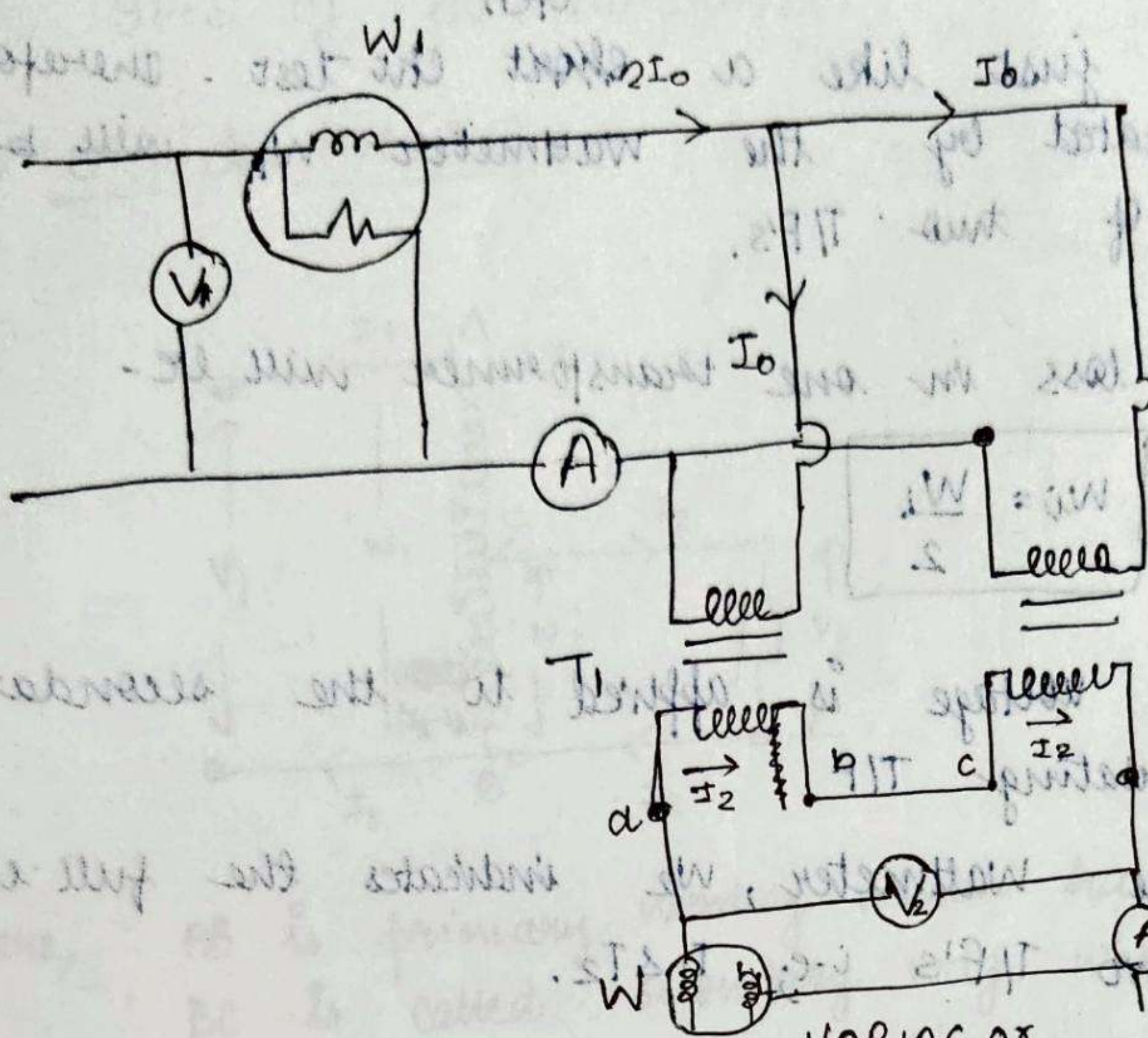- This is another for determining efficiency, regulation & heating of the T/F under load.
- In order to determine max temp rise it is necessary to conduct a full load test on a T/F. For this we need two identical T/F
- The primary wdgs of two T/F are connected in llr & rated voltage is applied on the primary side.




VARIAC or variable voltage

Case (i) - Same polarity

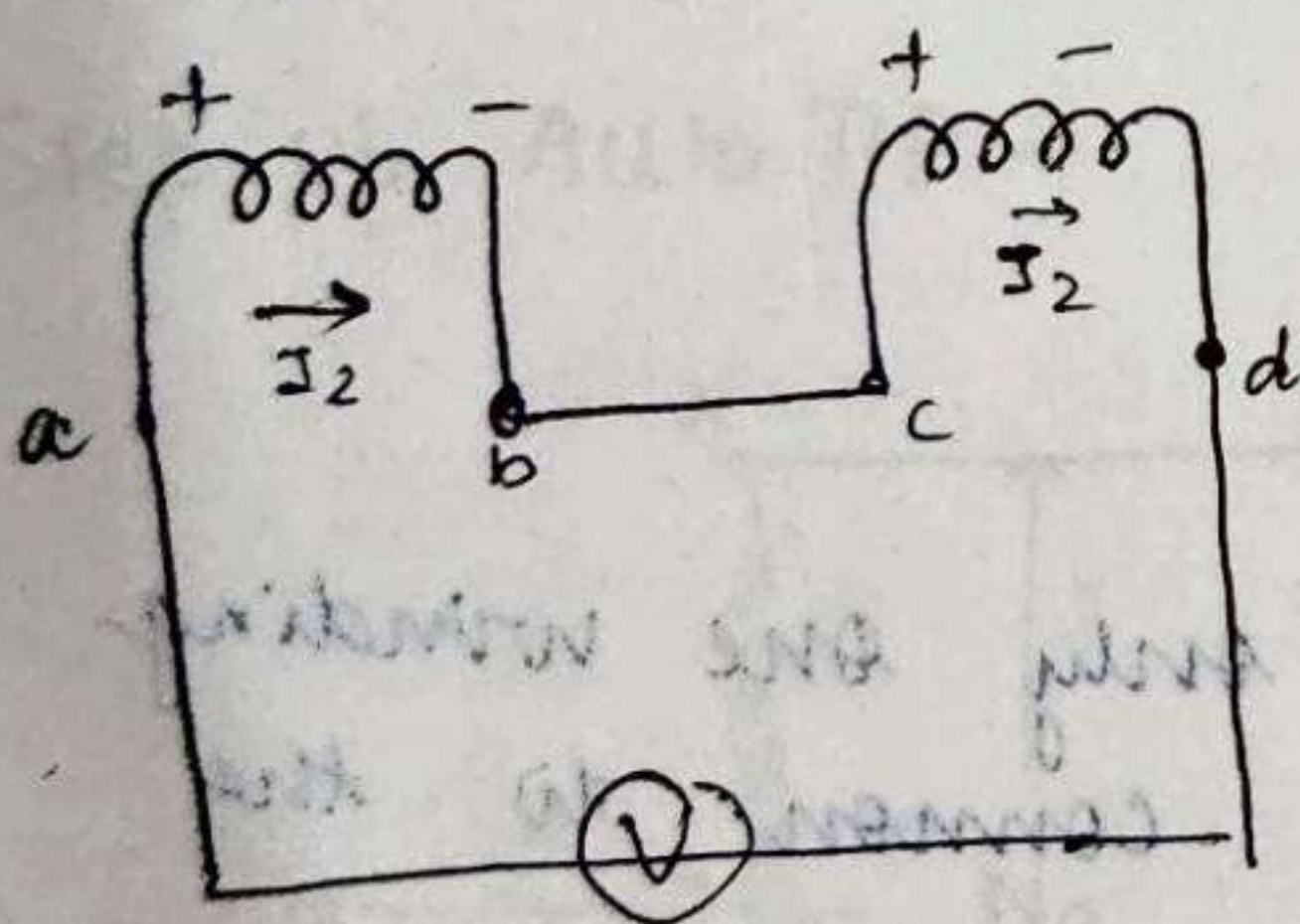

$$\text{Net current} = I_0 = I_1 + I_2$$

Case (ii) - Reverse polarity

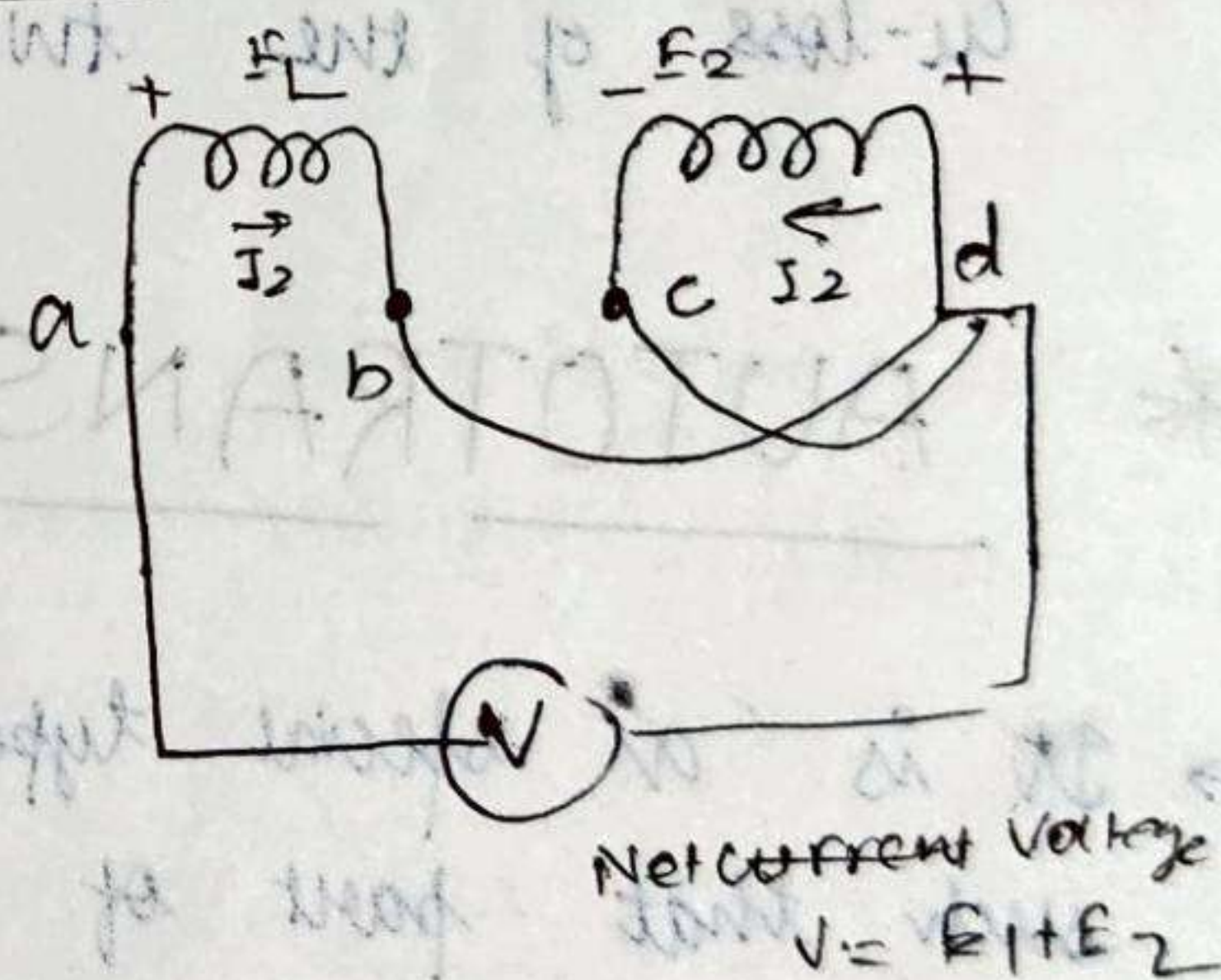

$$\text{Net current voltage } V = E_1 + E_2$$

→ The secondaries wdg are connected in series with their polarities in phase opposition. which is checked by voltmeter V_2 . When the secondary are in phase opposition voltmeter will read zero. and therefore there will be no current in secondaries of the two TIFs.

→ As there is no current in the secondaries, there will be no copper loss in the two transformers. Wattmeter W_2 reading will be zero.

→ This situation is just like a ^{open} short ckt test. Therefore, the losses integrated by the wattmeter W_1 will be the iron loss of two T/F's.

→ Therefore, iron loss in one transformer will be -

$$W_i = \frac{W_1}{2}$$

→ Now a small voltage is applied to the secondary ckt by a regulating T/F.

→ Reading of the wattmeter, W_2 indicates the full load Cu-loss of two T/F's i.e., T_1 & T_2 .

→ Only Cu-loss is determined because ↓

→ At low voltage iron losses are almost negligible. Therefore, the reading of wattmeter W_2 indicates only Cu-loss of the two T/F's.

* AUTOTRANSFORMER

⑦

→ It is a special type of T/F having only one winding such that part of the winding is common to the primary & secondary.


→ The two wdg's are electrically connected. This T/F works on the principle of both conduction & induction.

→ In this T/F, the part of power is ~~to~~ transferred conductively and inductively as well. Therefore, it's KVA rating is higher than two winding T/F.

→ It's efficiency is high and voltage regulation is low. as compared to two wdg T/F.

* Types of Autotransformer


(a) Step-down Auto T/F

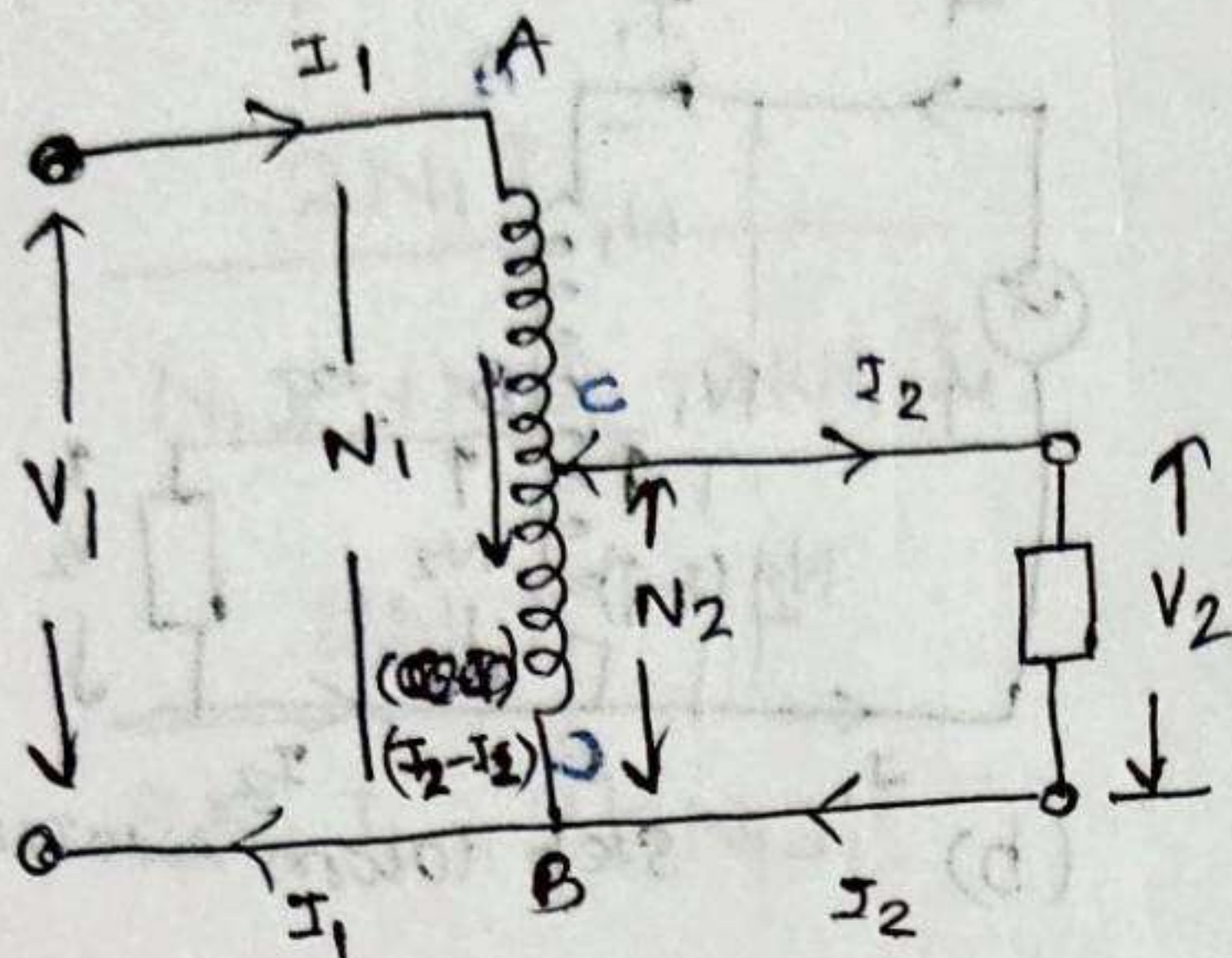

Here, AB is primary winding which has N_1 turns.
BC is called secondary wdg which has N_2 turns.

(b) Step-up Tran

(b) Step up Auto T/F

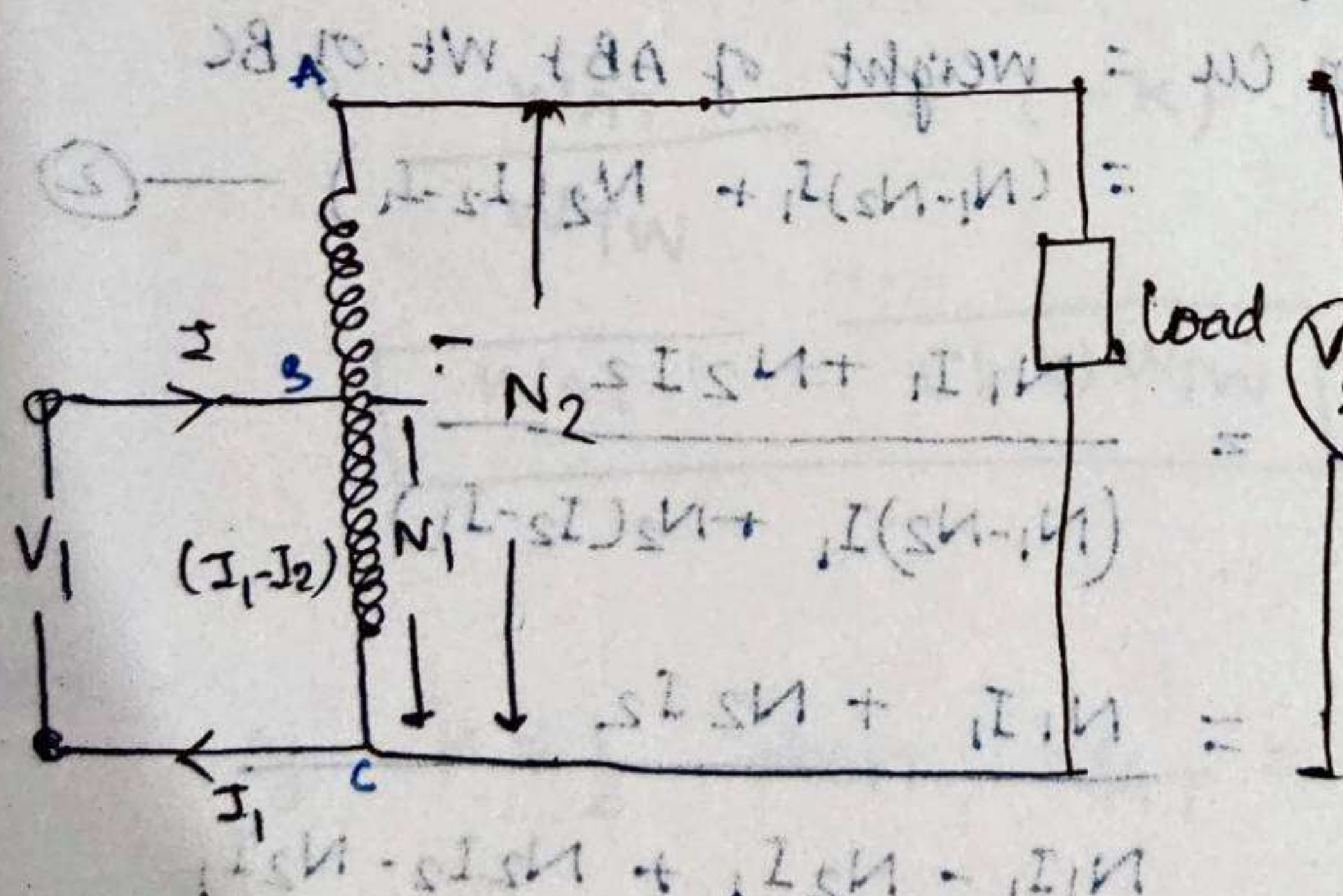

Here, $N_2 > N_1$


$V_2 > V_1$

$I_2 < I_1$


$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = K > 1$$

* SAVING OF COPPER IN AUTOTRANSFORMER -

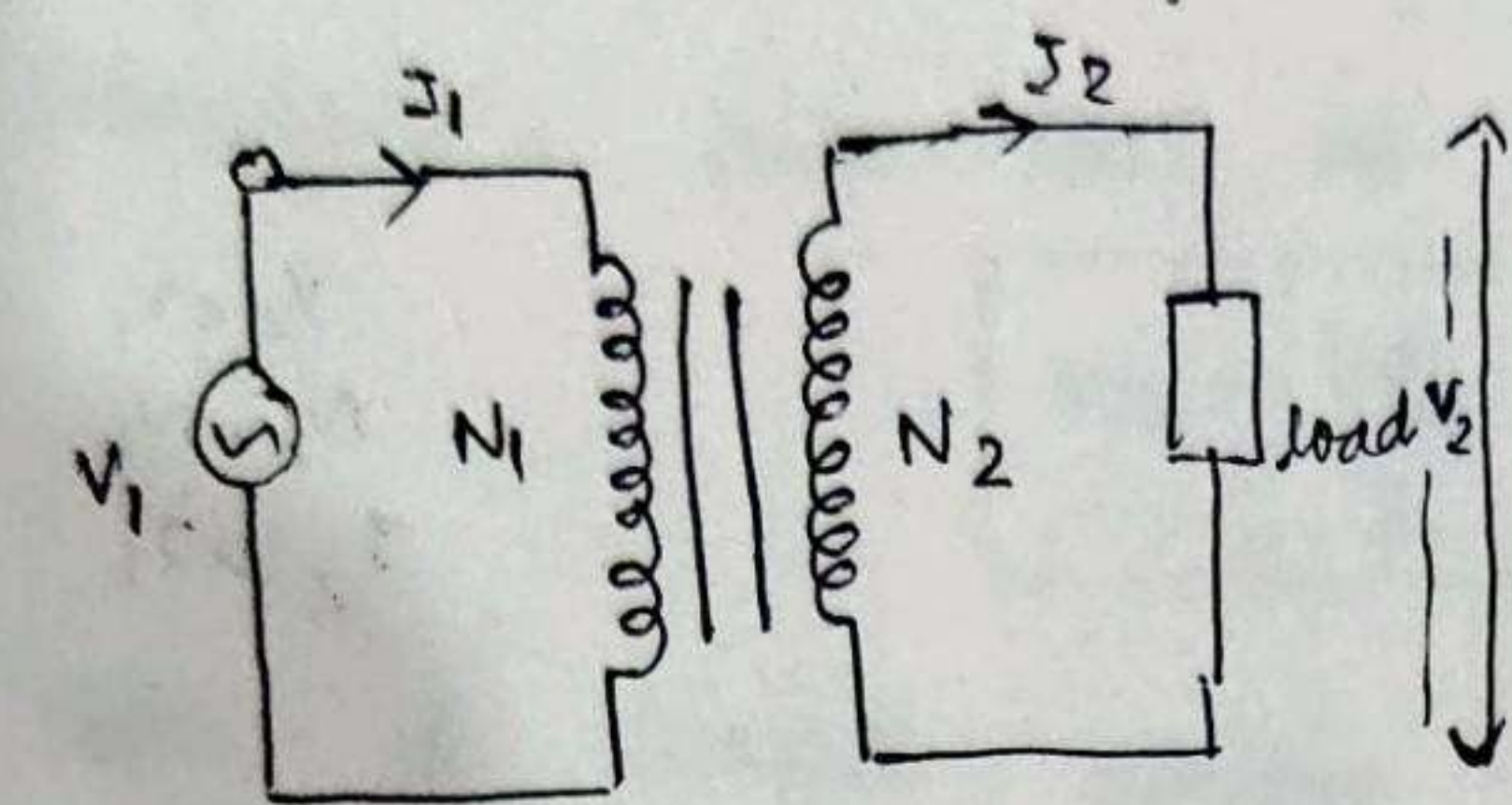Consider a two winding T/F and a stepdown auto T/F, as shown in given diagram.



(a) T/F - two wdg

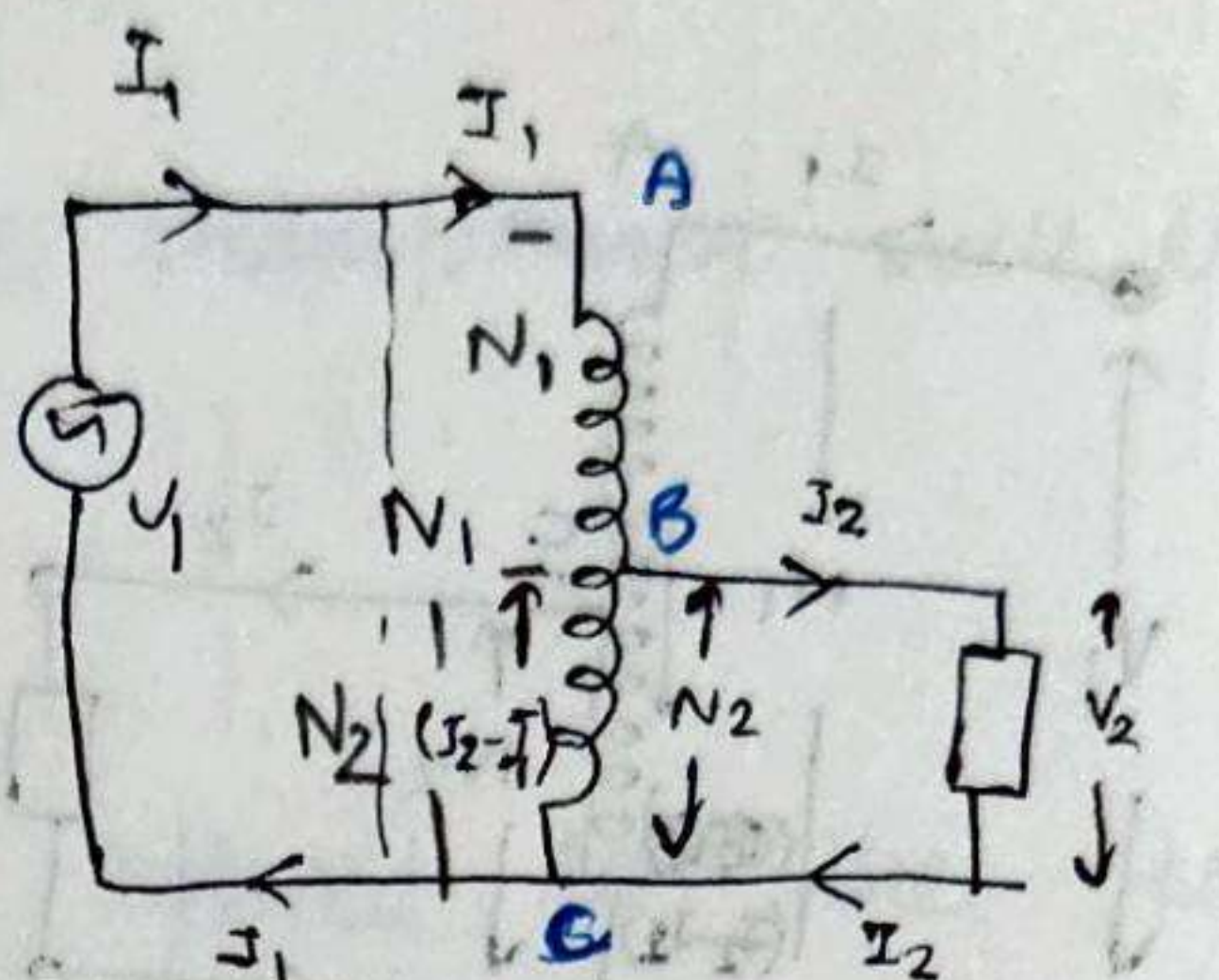

(b) Step down AutoT/F

$$V_2 < V_1 \\ I_2 > I_1$$

Note -

$$\text{wt of cu} = \text{Volume} \times \text{density}$$

$$\text{wt cu} = A l \rho$$

$$\therefore \text{wt of cu} \propto A \cdot l$$

$$\text{wt of cu} \propto I \cdot N$$

$$l \propto N$$

$$A \propto I$$

→ area of wire.

→ In two winding T/F, $\text{wt. of cu} = N_1 I_1 + N_2 I_2$ — (1)

→ In autotransformer, $\text{wt of cu} = \text{weight of AB} + \text{wt of BC}$
 $= (N_1 - N_2) I_1 + N_2 (I_2 - I_1)$ — (2)

Now,

$$\frac{\text{Wt of two wdg T/F}}{\text{Wt of Auto T/F}} = \frac{N_1 I_1 + N_2 I_2}{(N_1 - N_2) I_1 + N_2 (I_2 - I_1)}$$

$$= \frac{N_1 I_1 + N_2 I_2}{N_1 I_1 - N_2 I_1 + N_2 I_2 - N_2 I_1}$$

$$= \frac{N_1 I_1 + N_2 I_2}{N_1 I_1 + N_2 I_2 - 2 N_2 I_1} \quad (3)$$

We know

$$\frac{N_2}{N_1} = K = \frac{I_1}{I_2}$$

$$N_2 I_2 = N_1 I_1$$

$$\therefore N_2 = K N_1$$

Putting $N_1 I_1$ in eq (3)

$$\Rightarrow \frac{N_1 I_1 + N_1 I_1}{N_1 I_1 + N_1 I_1 - 2N_1 I_1} \quad \therefore N_2 = KN_1$$

$$\Rightarrow \frac{2N_1 I_1}{N_1 I_1 + N_1 I_1 - 2KN_1 I_1}$$

$$\Rightarrow \frac{2N_1 I_1}{2N_1 I_1 - 2KN_1 I_1}$$

$$\Rightarrow \frac{2N_1 I_1}{2N_1 I_1 (1-K)}$$

$$\Rightarrow \frac{1}{1-K}$$

So, $\frac{W_t \text{ of two wdg T/F}}{W_t \text{ of auto T/F}} = \frac{1}{1-K}$


$$\frac{W_{AT}}{W_{TW}} = (1-K)$$

$$W_{AT} = (1-K) W_{TW}$$

Note-


If $K = \frac{1}{2}$ then $W_{AT} = \frac{1}{2} W_{TW}$

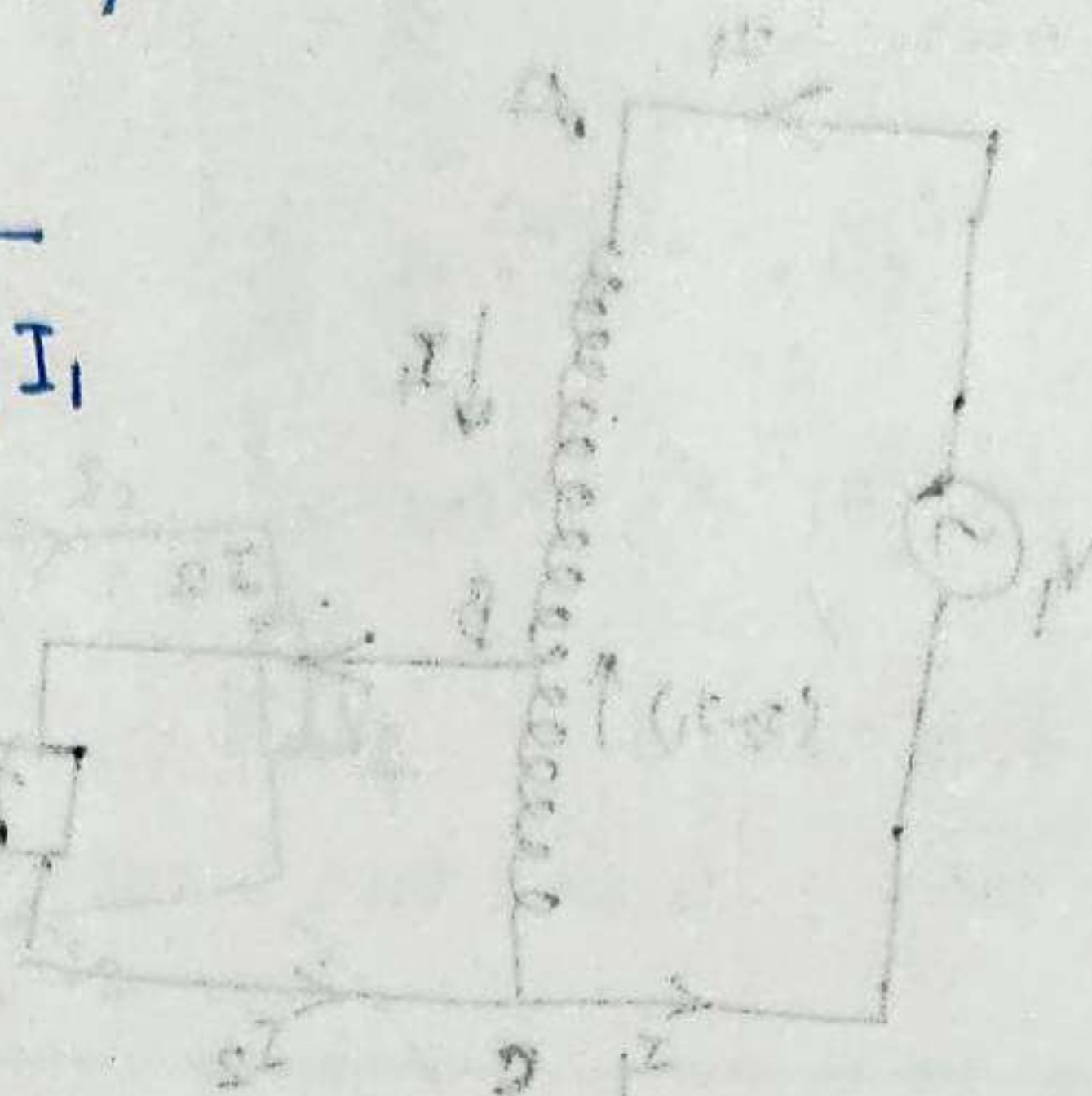- * Amount of volt and ampere in load $\rightarrow$ Rating of T/F (kVA)
Capacity of T/F or V multiply by Ampere $\rightarrow$ known as kVA rating.
- * Small T/F $\rightarrow$ rating $\rightarrow$ VA
- * Big T/F $\rightarrow$ " $\rightarrow$ kVA ($K=10^3$) = 10^3 VA
- * Biggest T/F $\rightarrow$ " $\rightarrow$ MVA ($M=10^6$) = 10^6 VA.



* POWER TRANSFER IN AUTO TRANSFORMER -

Consider a step-down auto-transformer.

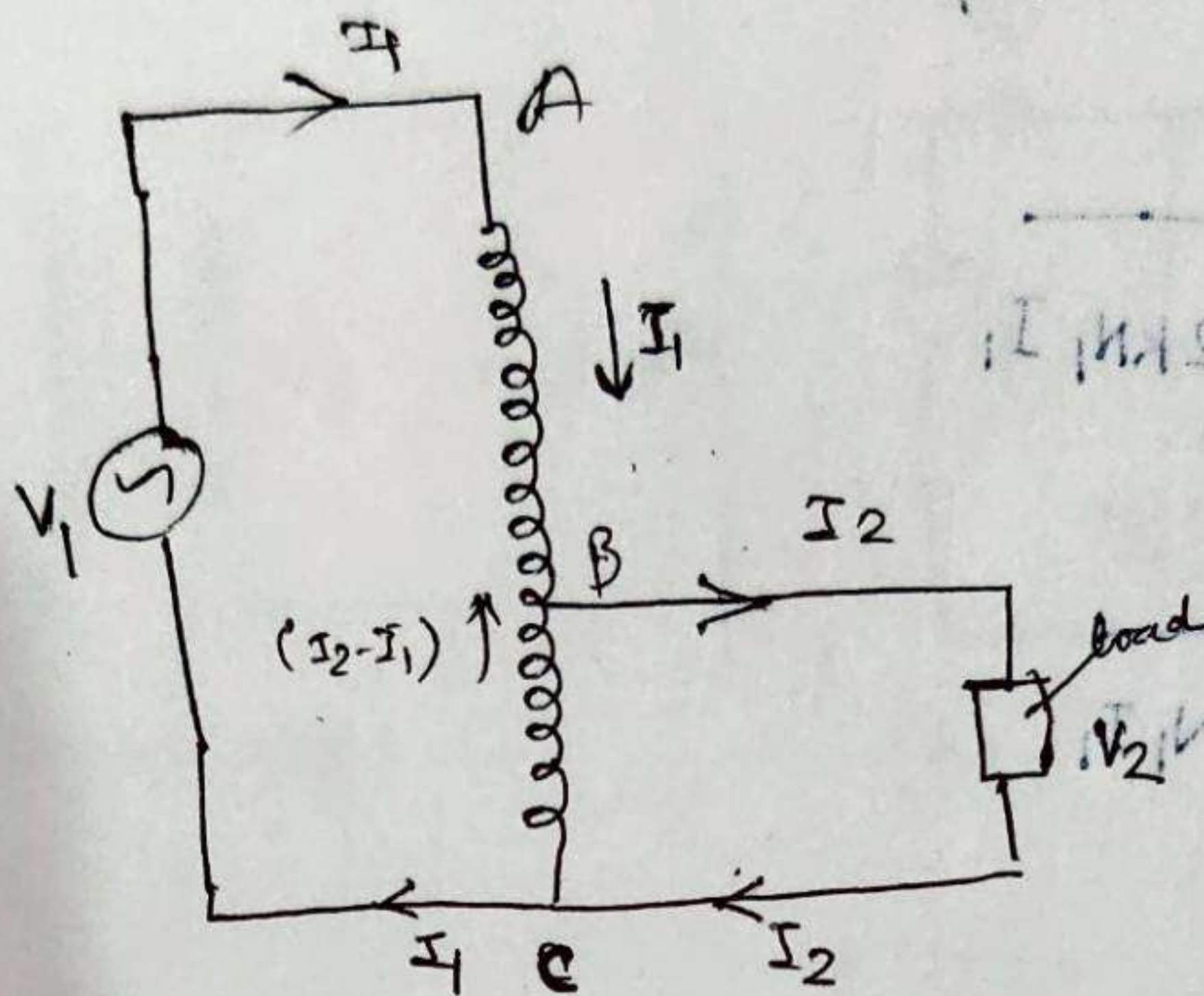

Here, $I_2 > I_1$ ($\therefore$ step down AUTO T/F ($\uparrow$ Current $\downarrow$ V))

→ Power transferred inductively (through T/F action)

P_t = Power in secondary wdg.

$$= V_2 (I_2 - I_1)$$

$$= V_2 I_2 - V_2 I_1$$

$$= V_1 I_1 - (K V_1) I_1$$

$$P_t = V_1 I_1 (1 - K)$$

$$\therefore P_{in} = V_1 I_1$$

$$P_t = (1 - K) P_{in}$$

$$P_t = P_{in} - K P_{in}$$

$$P_{in} = P_t + K P_{in}$$


Where, P_t = inductively transferred

P_c = conductively transferred

$$P_{in} = P_t + P_c$$

* VA RATING OF AUTOTRANSFORMER-

Consider a step-down AUTO T/F

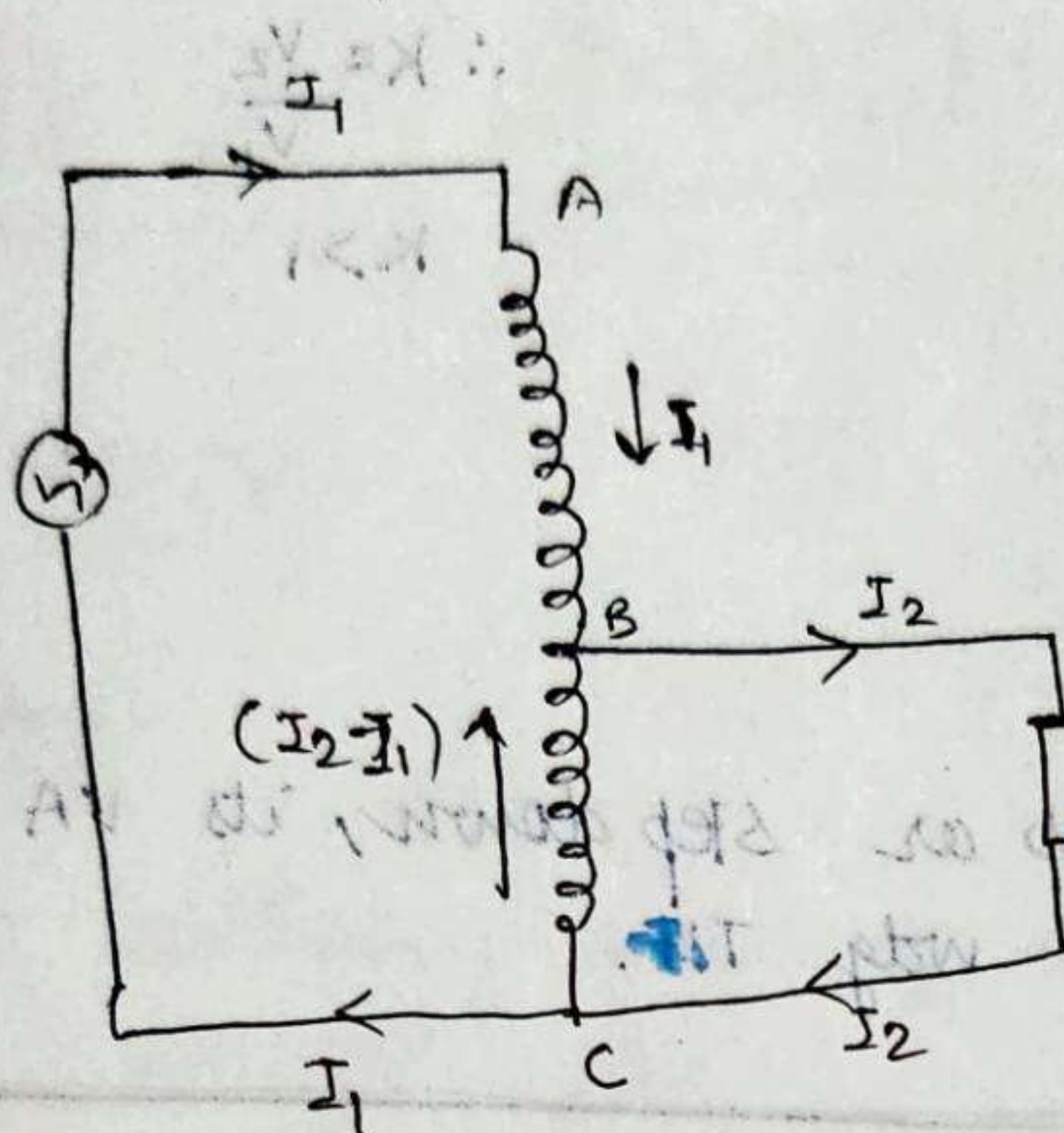

$$(VA)_{AT} = V_1 I_1$$


$$(VA)_{AT} > (VA)_{TW}$$

$$(VA)_{AT} < (VA)_{TW}$$

• VA rating of stepdown auto T/F

$$(VA)_{AT} = V_2 I_2$$

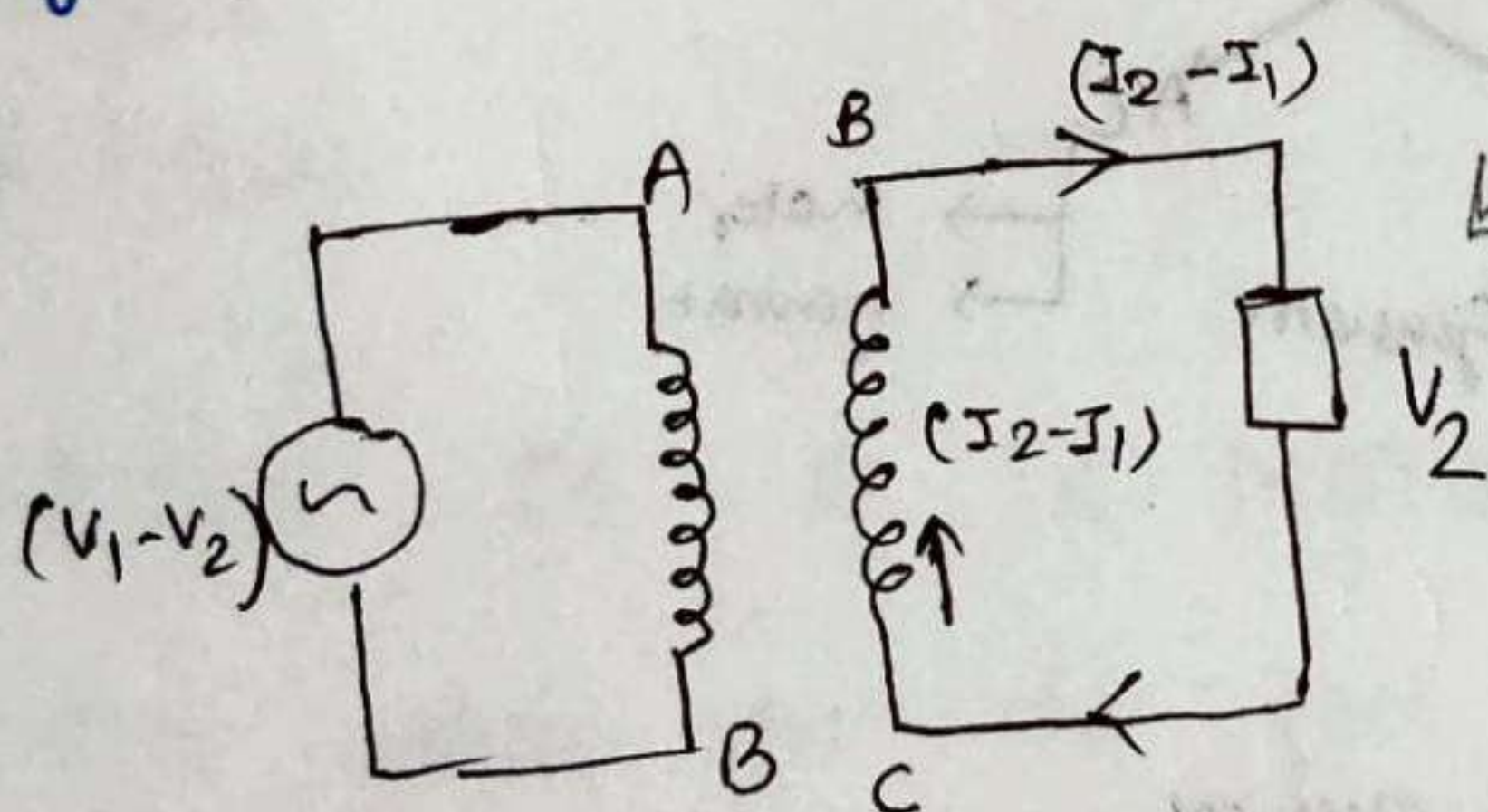• If this Auto transformer is converted into two winding T/F with primary as AB & secondary as BC.



Stepdown AT/F breaks into two parts to form a new T/F

• NOW VA rating of this two wdg T/F

$$(VA)_{TW} = V_2 (I_2 - I_1)$$

$$= V_2 I_2 - V_2 I_1$$

$$= V_1 I_1 - k V_1 I_1$$

$$= (1 - k) V_1 I_1$$

$$(VA)_{TW} = (1 - k) (VA)_{AT}$$

$$\therefore k = \frac{N_2}{N_1} \Rightarrow N_2 < N_1$$

So, $(VA)_{TW} < (VA)_{AT}$, as $k < 1$

OR

$$(VA)_{AUTOTIF} > (VA)_{TW}$$

→ Autotransformers is better because it have more VA rating